

Circuit Elements

Electric Charge and Current

- The most basic quantity in an electric circuit is the **electric charge**.
- We all experience the effect of electric charge when we try to **remove our wool sweater** and have it stick to our body or walk across a carpet and receive a shock.

Charge is an electrical property of the atomic particles of which matter consists, measured in **coulombs** (C).





➤ The following points should be noted about electric charge:

- 1) The coulomb is a large unit for charges. In 1 C of charge, there are 6.24×10^{18} electrons. Thus realistic or laboratory values of charges are on the order of pC, nC, or μC .
- 2) According to experimental observations, the only charges that occur in nature are integral multiples of the electronic charge $e = -1.602 \times 10^{-19}\text{ C}$.
- 3) The *law of conservation of charge* states that charge can neither be created nor destroyed, only transferred. Thus the algebraic sum of the electric charges in a system does not change.

Circuit Elements


What is an electric circuit?

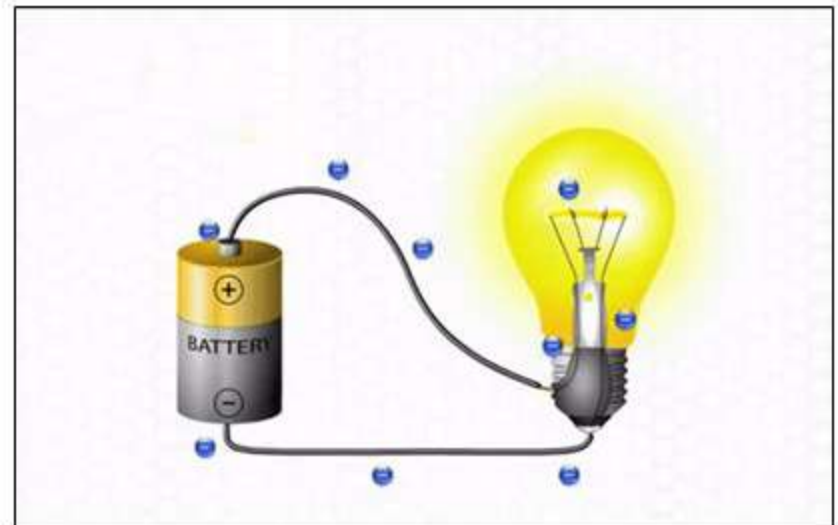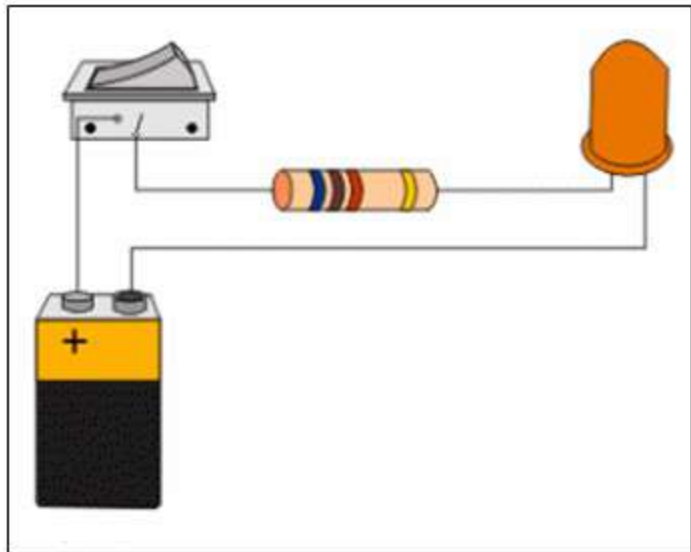- It is a **closed path** for transmitting an electric current through the medium of **electrical and magnetic fields**.
- The flow of electrons across the loop constitutes the electric current.
- Electrons enter the circuit through the 'Source' which can be a **battery or a generator**.



Circuit Elements

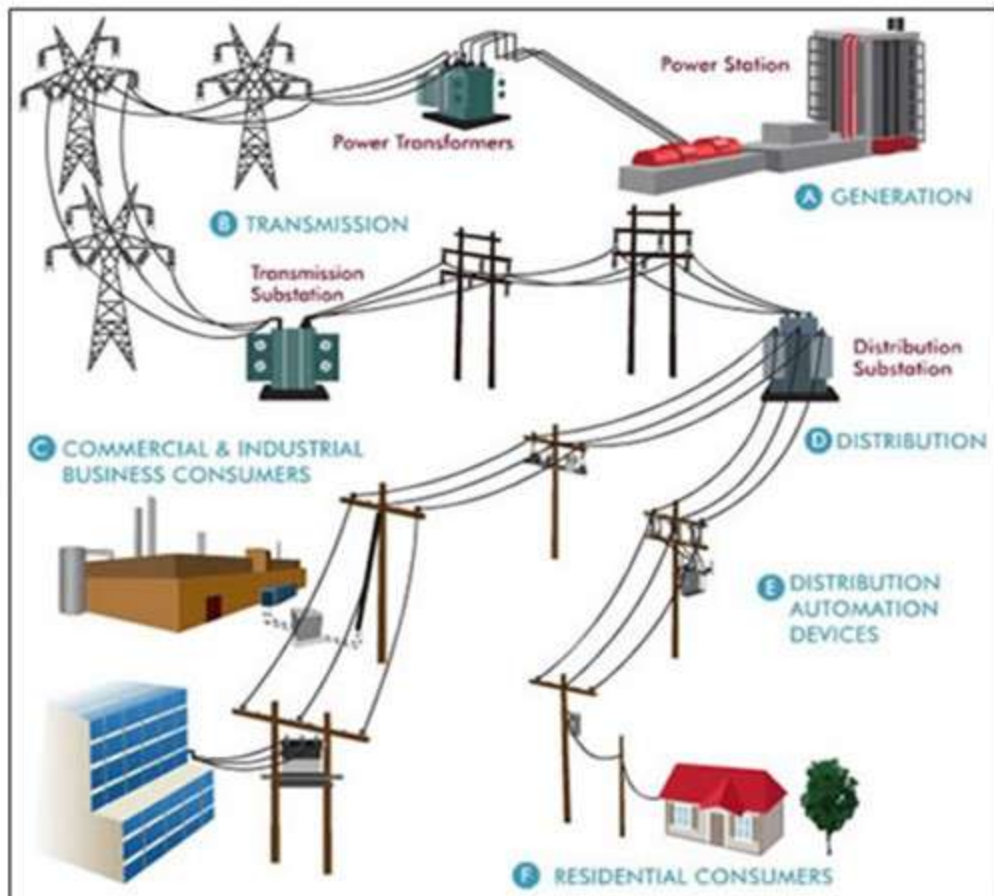Electrical Network: A combination of various electric elements (Resistor, Inductor, Capacitor, Voltage source, Current source) connected in any manner.



Circuit Elements

Circuit Elements

Active Elements


- Active Elements are those which can generate energy.
- Batteries, generators, operational amplifiers and diodes.
- The source elements are the most significant active elements.

Passive Elements

- Passive Elements can be defined as elements which can control the flow of electrons through them.
- Resistor, inductor, capacitor.
- They either increase or decrease the voltage.


Circuit Elements

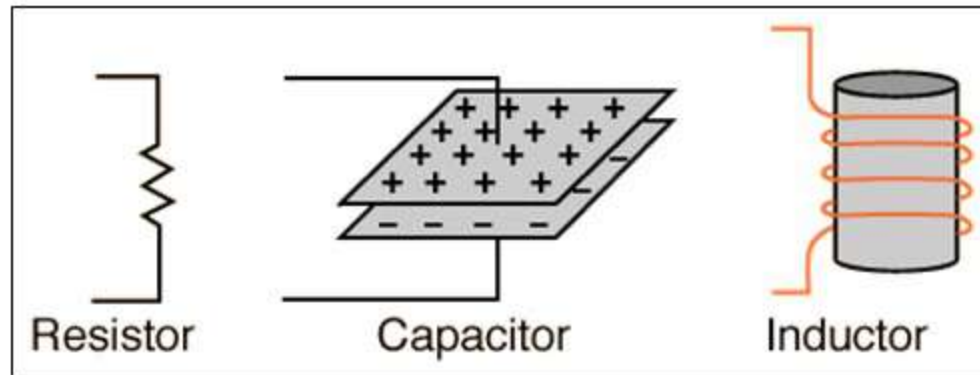➤ **Passive Element:** The element which receives energy (or absorbs energy) and then either converts it into **heat (R)** or stored it in an **electric (C)** or **magnetic (L)** field is called passive element.




Circuit Elements

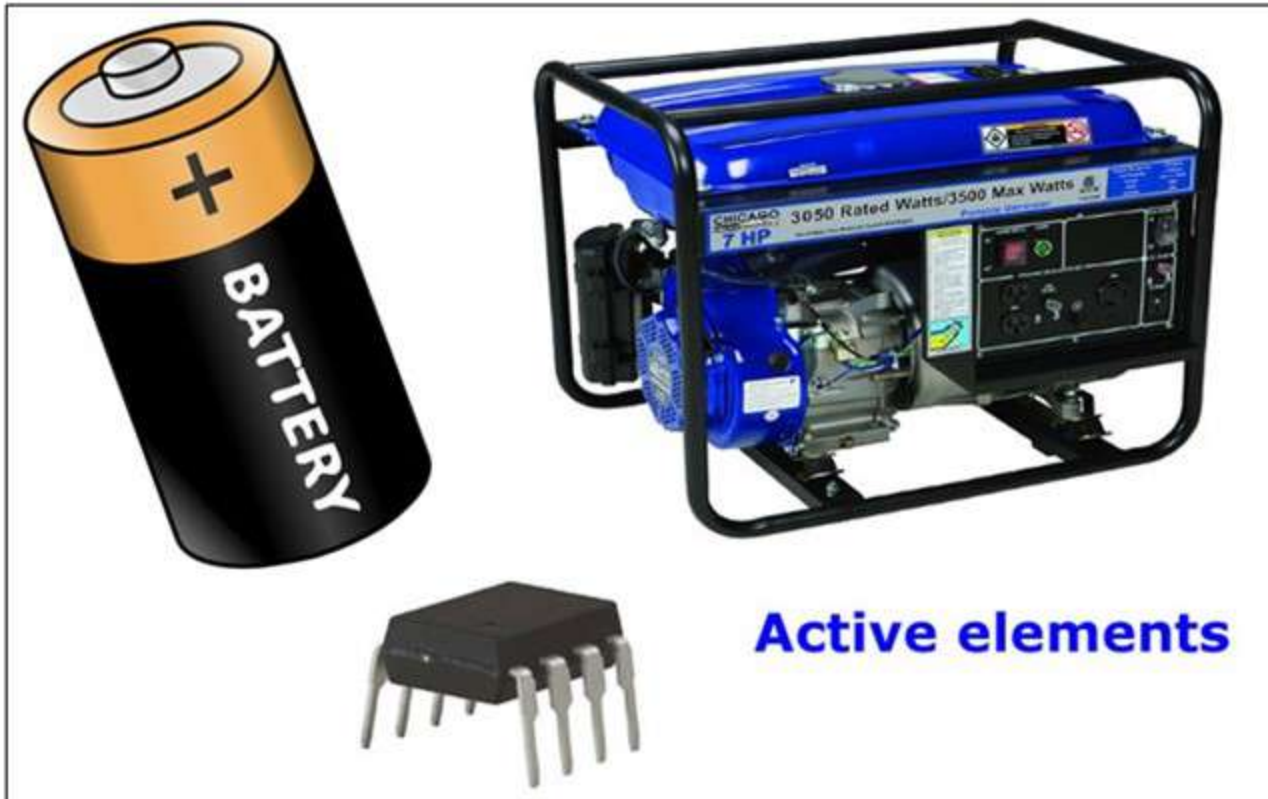➤ **Active Element:** The elements that supply energy to the circuit is called active element. Examples of active elements include voltage and current sources, generators and electronic devices that require power supplies.





Circuit Elements

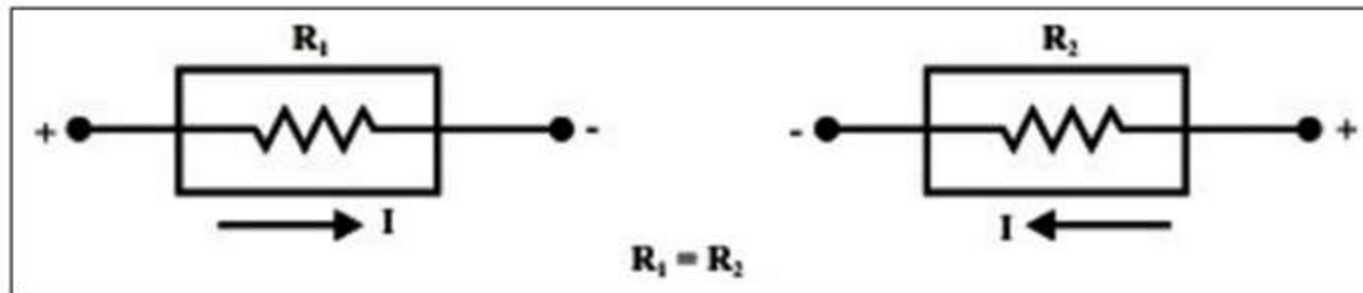➤ **Bilateral Element:** Conduction of current in both directions in an element (example: **Resistance; Inductance; Capacitance**) with same magnitude is termed as bilateral element.



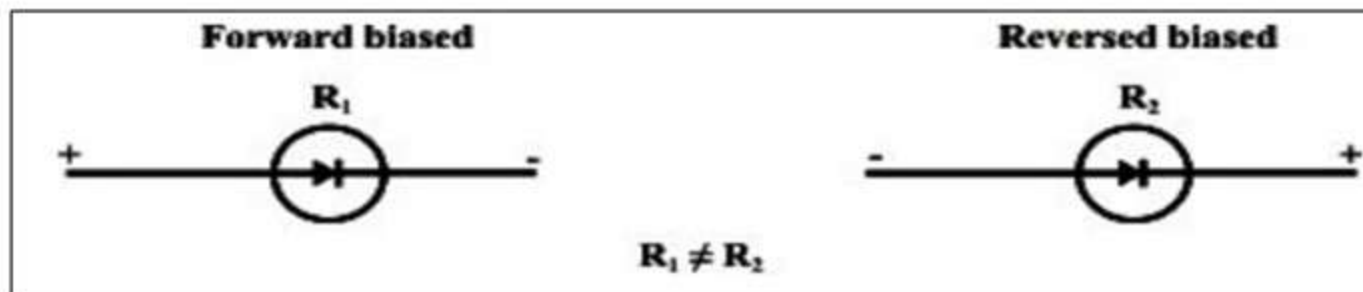➤ **Unilateral Element:** Conduction of current in one direction is termed as unilateral (example: Diode, Transistor) element.



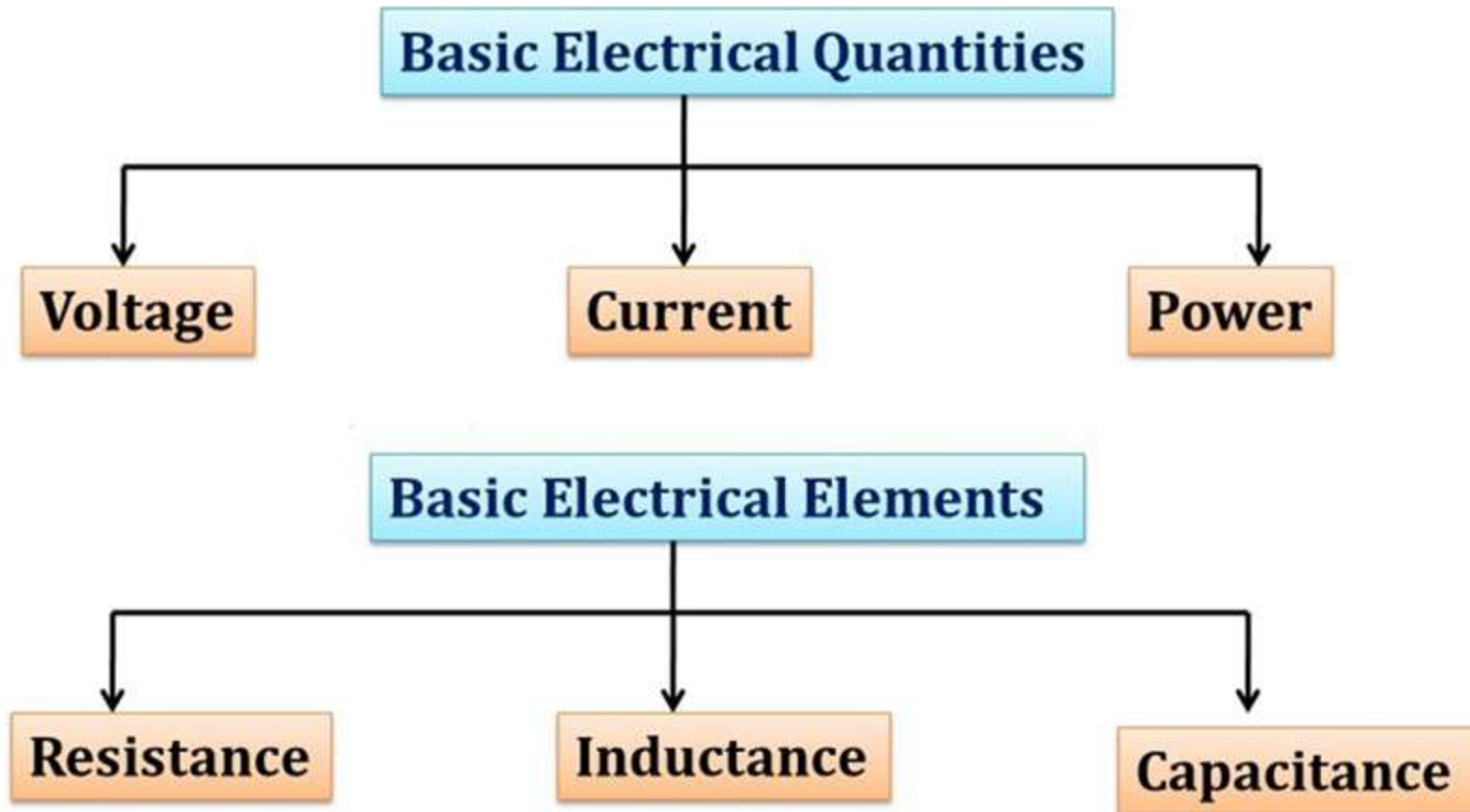

Circuit Elements: Voltage


- Voltage is the difference in electric potential between two points.
- Voltage is also called an electromotive force (e.m.f).
- When **1 J** of work is required to move **1 C** of charge from **A** to **B**, there is a voltage of **1 volt** between **A** and **B**.
- Voltage (**V** or **v**) across an element requires both a magnitude and a polarity.
- It is measured in volts.

Alessandro Volta



Circuit Elements: Current

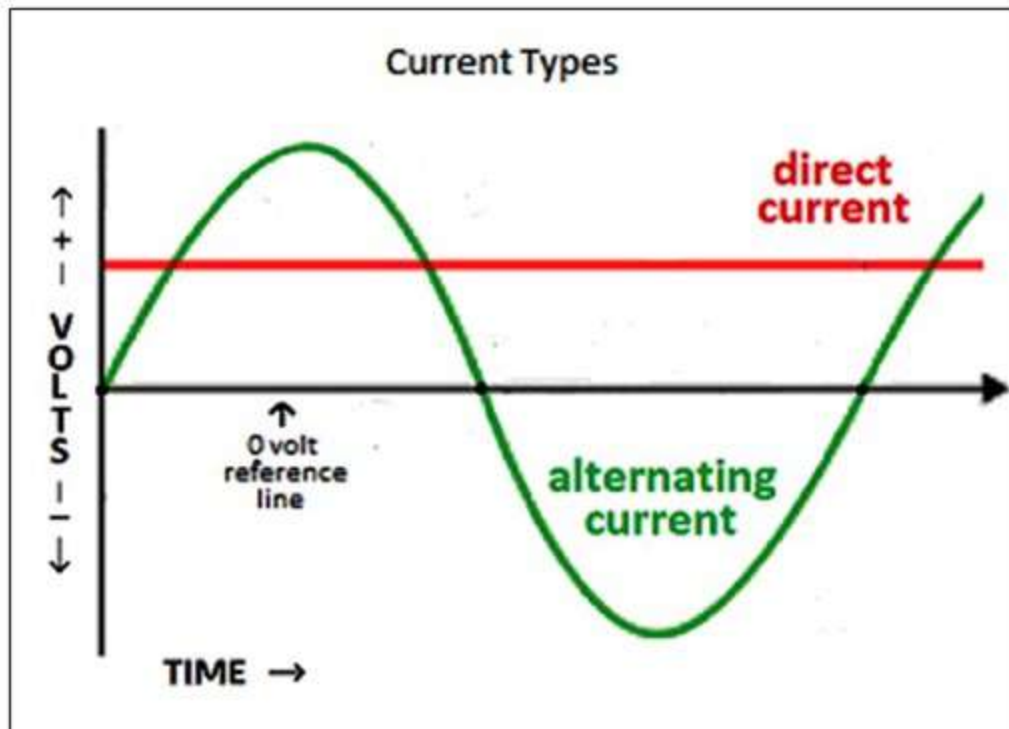- The unit of current is the ampere (A).
- We note that, 1 ampere = 1 coulomb/second
- We normally refer to current as being either **direct (DC)** or **alternating (AC)**.



1775-1836
Andre-Marie Ampere

Circuit Elements: Power

- Electric power is the rate at which electrical energy is transferred by an electric circuit.
- The SI unit of power is the watt, one joule per second.
- Electric power is usually produced by generators, but can also be supplied by sources such as batteries.
- Electric power is usually sold by the kilowatt-hour (3.6 MJ-1 unit).
- Electric utilities measure power using an electricity meter, which keeps a running total of the electric energy delivered to a customer.





1736 - 1819

James Watt

Circuit Elements: Resistor


Resistance (R)

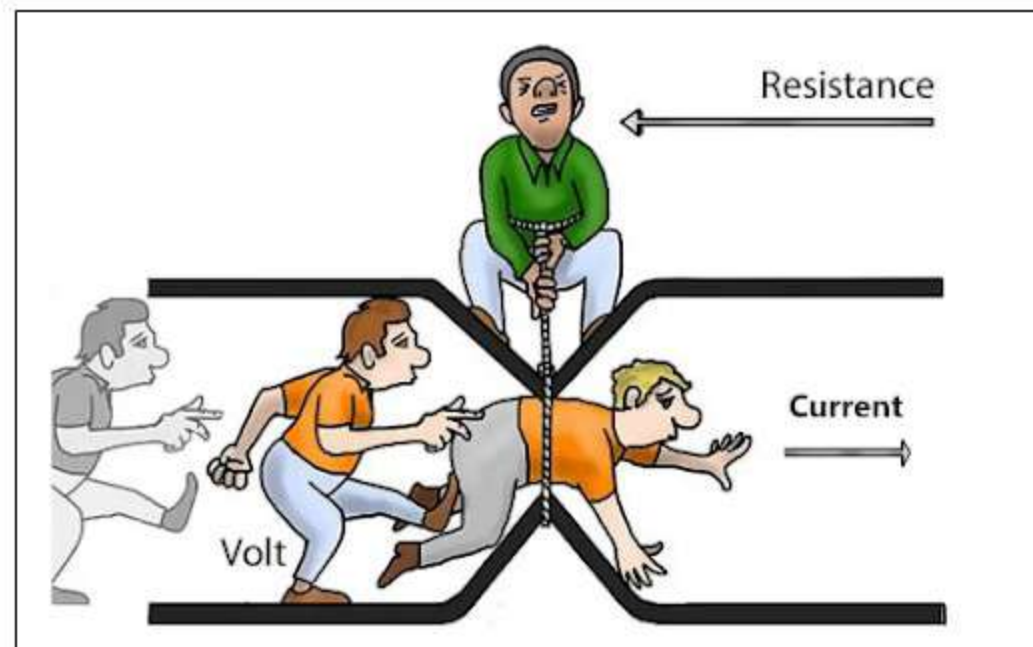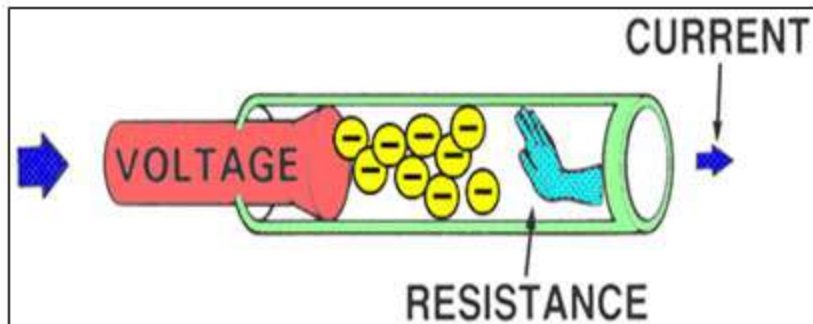- Resistance is a “**property**” of material **which opposes** the flow of electricity through it when potential is applied.



Circuit Elements: Resistor

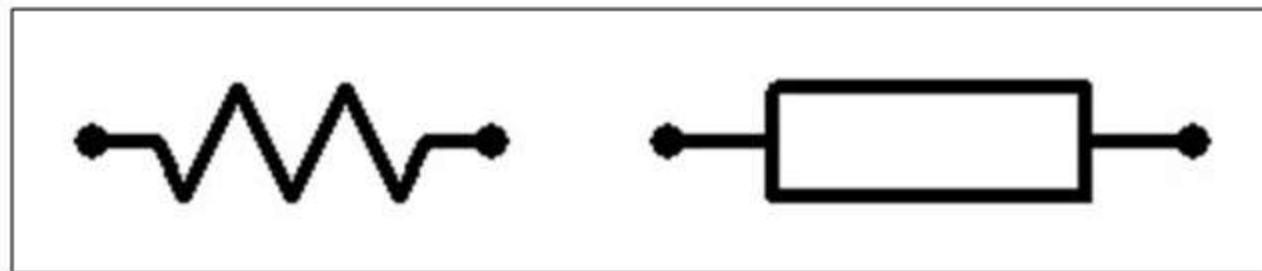- It opposes the flow of electrons (**current**).




- Resistance is measured in units called “Ohm”, symbol is Ω .

$$R = \frac{V}{I}$$
$$R = \frac{\rho l}{a}$$



1789-1854
George-Simon Ohm

Circuit Elements: Resistor

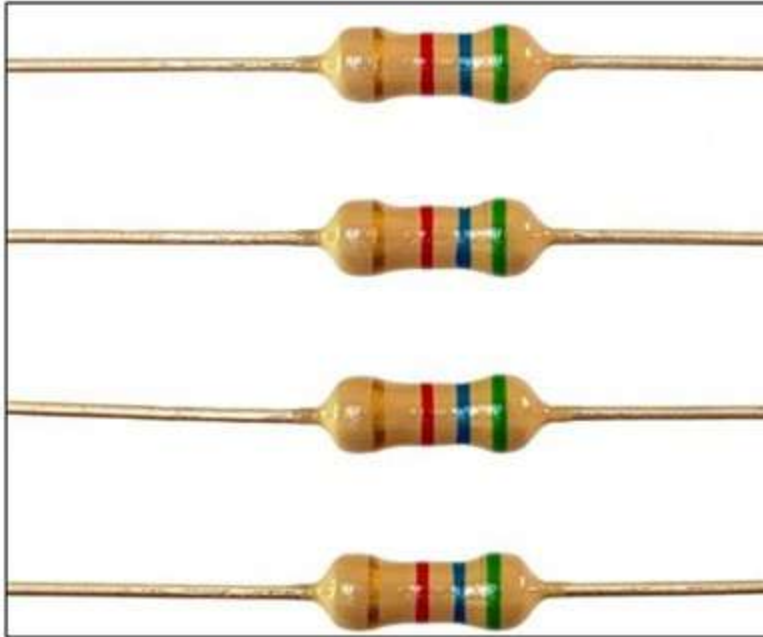



Fixed Resistor



Variable Resistor


Circuit Elements: Resistor

Common Fixed Resistors

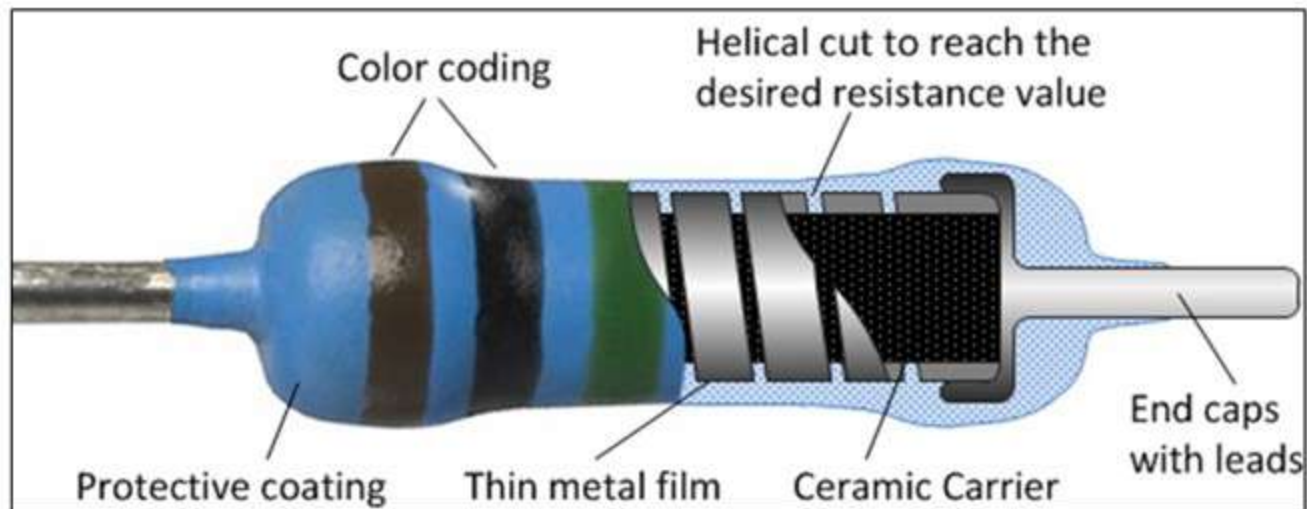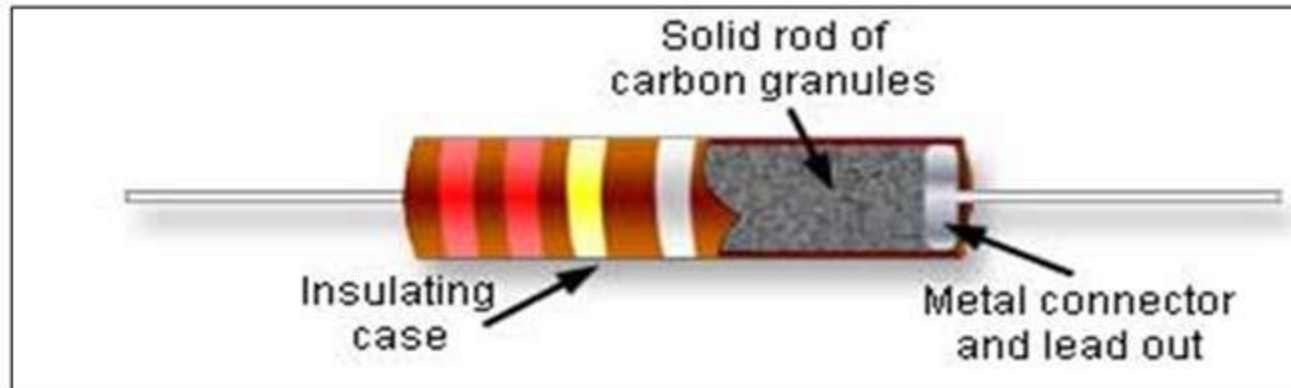

Circuit Elements: Resistor

Color-code Bands on a Resistor

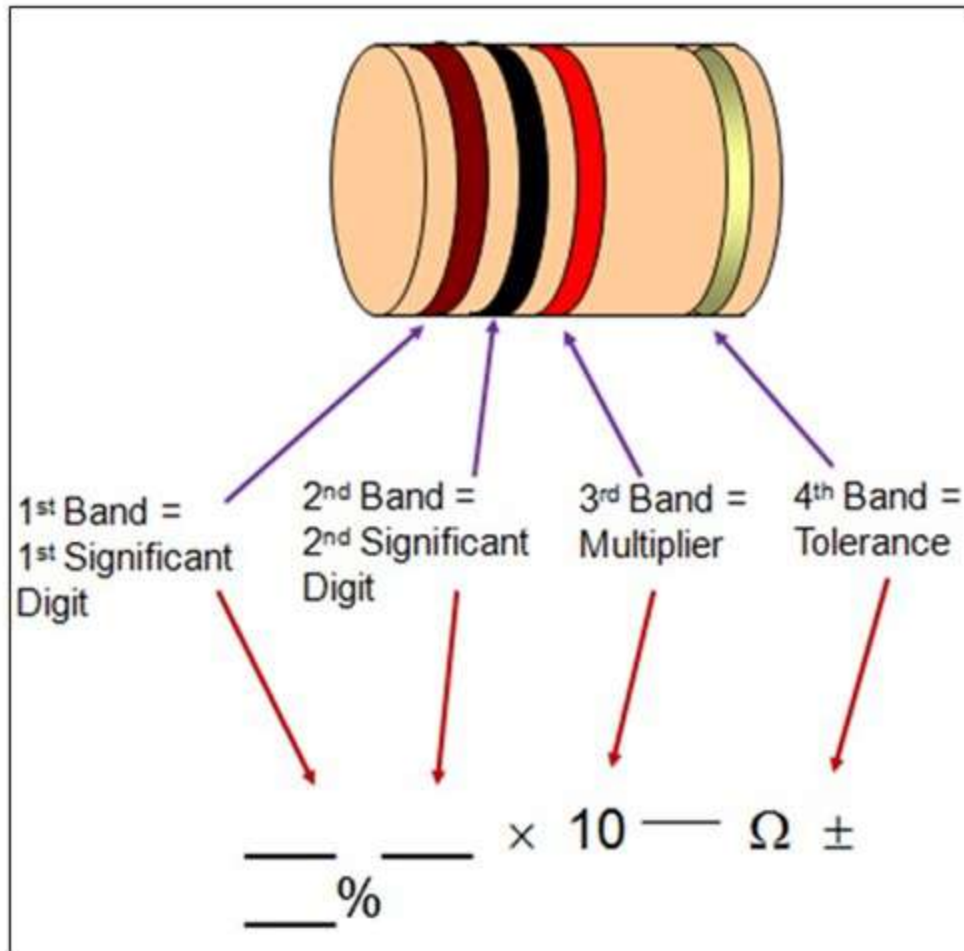


Number	Color
0	Black
1	Brown
2	Red
3	Orange
4	Yellow
5	Green
6	Blue
7	Violet
8	Gray
9	White

±5% (0.1 multiplier if 3rd band)	Gold
±10% (0.01 multiplier if 3rd band)	Silver

Circuit Elements: Resistor

- One way to calculate resistance is

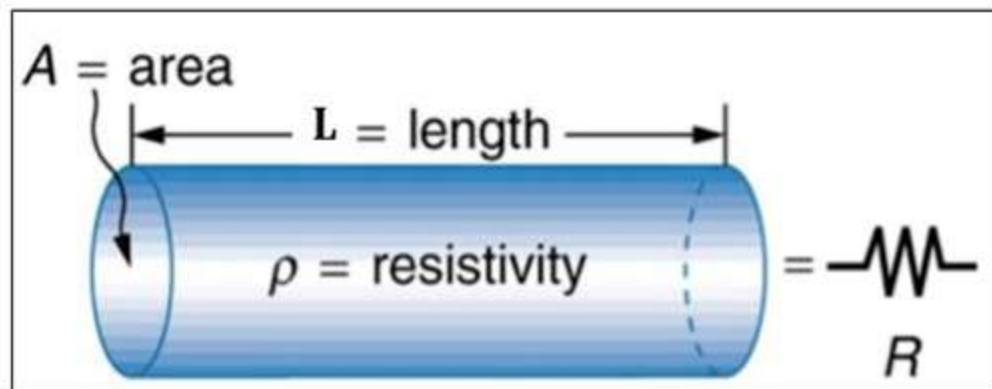

$$R = \rho \frac{L}{A}$$

ρ : Resistivity or specific resistance of the material

L: Length of the conductor


A: Area of the conductor

- Another form to calculate the resistance is applying **Ohm's law**.


Circuit Elements: Resistor

➤ Factors that affect the resistance:

Length

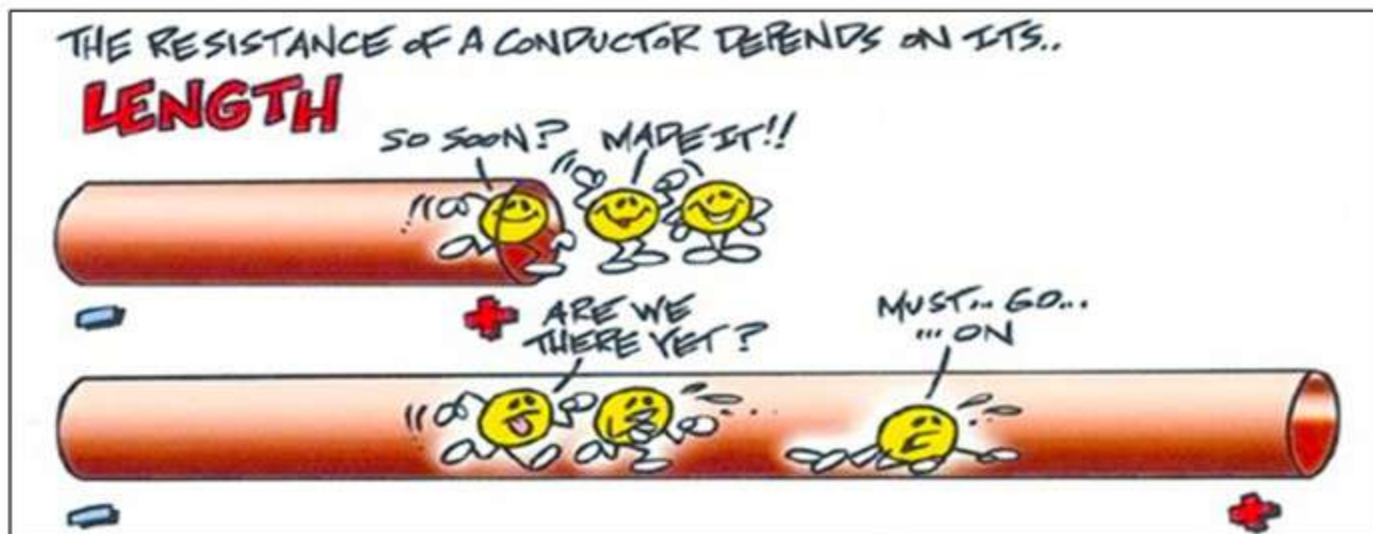

Thickness & Temperature

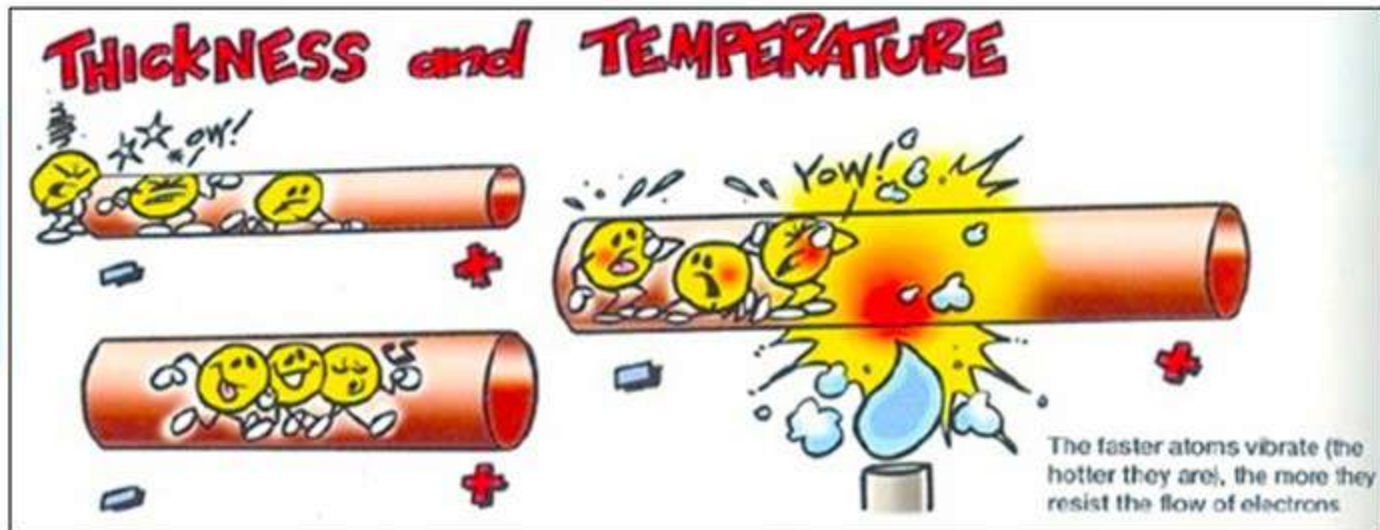

Ohm's Law

- **Georg Simon Ohm** (1787–1854), a German physicist, is credited with finding the relationship between current and voltage for a resistor.
- This relationship is known as **Ohm's law**.

Ohm's law states that the current flowing between two points of the circuit is directly proportional to the potential difference between the points.

$$i \propto v$$

$$i = \frac{1}{R} v$$





$$v = iR$$

Ohm defined the constant of proportionality for a resistor to be the resistance, **R**.

Inductance (L)

- An **inductor** is a passive electric component that stores energy in the form of a magnetic field.
- In its simplest form, an inductor consists of a wire loop or coil.

Inductor schematic symbol:

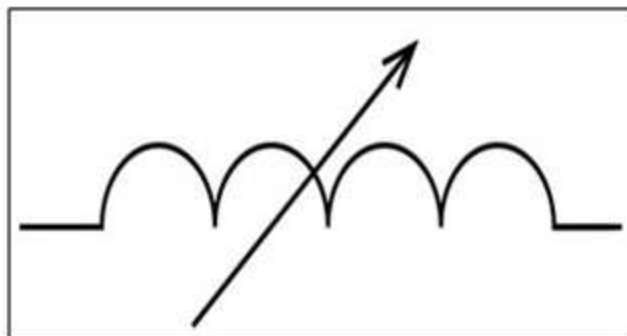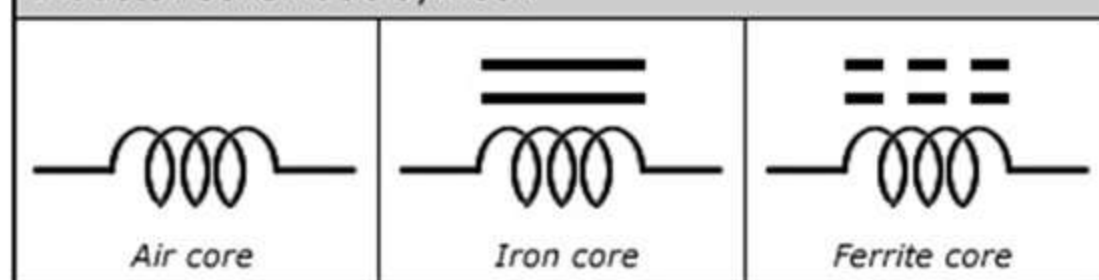

- The inductance is **directly proportional to the number of turns** in the coil.
- Inductance also **depends on the radius of the coil** and on the **type of material** around which the coil is wound.

Circuit Elements: Inductor



Circuit Elements: Inductor

- The standard unit of inductance is the **henry**, abbreviated H.
- More common units are the **microhenry**, abbreviated μH ($1 \mu\text{H} = 10^{-6} \text{ H}$) and the **millihenry**, abbreviated **mH** ($1 \text{ mH} = 10^{-3} \text{ H}$).
- It is commonly used in
 - ❖ Choke,
 - ❖ Filter,
 - ❖ Buck/Boost Regulator,
 - ❖ Reactive Power Compensation, etc.




1797-1878
Joseph Henry

Circuit Elements: Capacitor

Capacitance (C)

- The function of the **capacitor** is to store electric charge or in effect electrical energy.
- It is also known as **condenser**.
- The forms of practical capacitors vary widely, but all contain at least two conducting plates separated by a dielectric material.
- A dielectric can be **glass, ceramic, plastic film, air, vacuum, paper, mica, oxide layer** etc.


$$C = \frac{Q}{V}$$

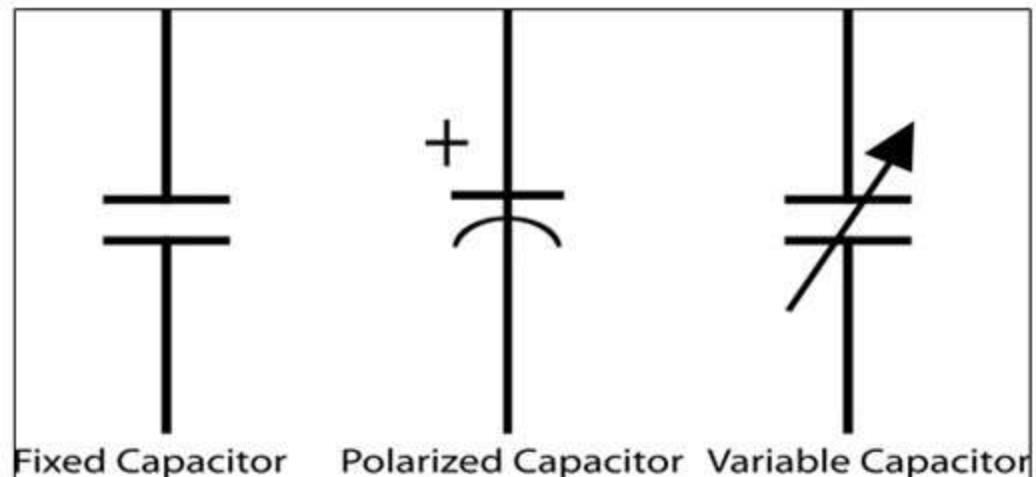

Circuit Elements: Capacitor



Ceramic Capacitor

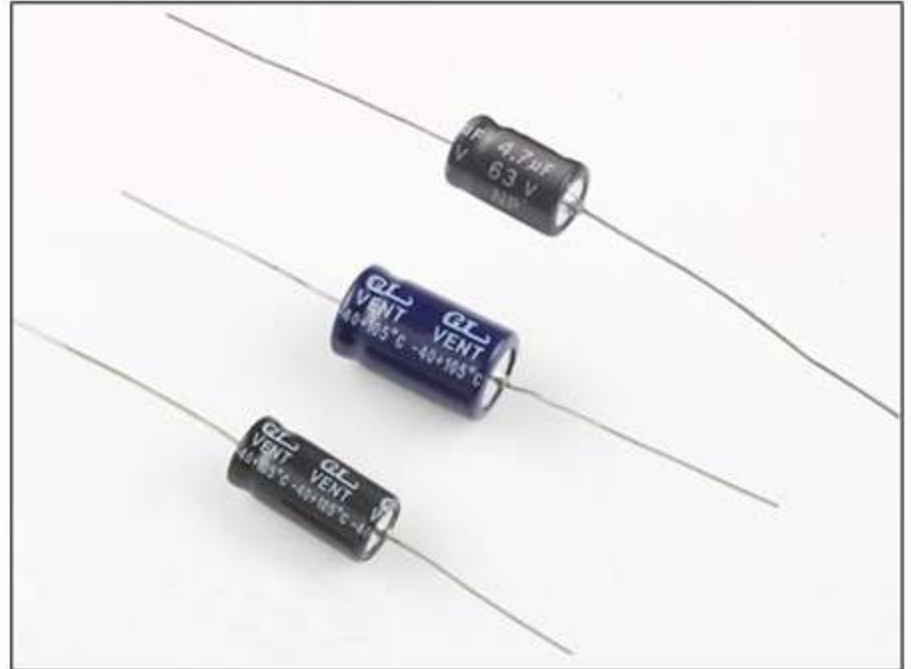

Electrolytic Capacitor

Circuit Elements: Capacitor

➤ Capacitance is a measure of the capacity of storing electric charge for a given potential difference.


➤ The SI unit of capacitance is the farad (F).

$$1 \text{ F} = 1 \text{ farad} = 1 \text{ coulomb/volt} = 1 \text{ C/V}$$

➤ A typical capacitance is in the **picofarad (pF)** to **millifarad (mF)** range.

➤ It is commonly used in

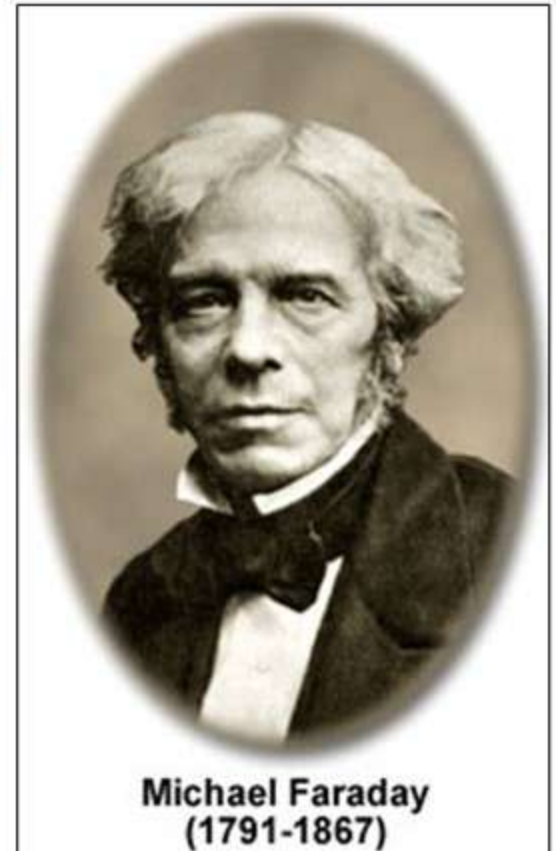- ❖ Storing energy,
- ❖ Power factor correction,
- ❖ Reactive power compensation,
- ❖ Starting single phase motors, etc.



- A **voltage source**, such as a **battery or generator**, provides a potential difference (voltage) between two points within an electrical circuit allowing current to flow around it.

The voltage can exist without current.

- The types of voltage source:

1) Independent Voltage Source:

- Direct Voltage Source
- Alternating Voltage Source

2) Dependent Voltage Source:

- Voltage Controlled Voltage Source
- Current Controlled Voltage Source.

Voltage Source


Independent Voltage Source

- The voltage source which can deliver **steady voltage** (fixed or variable with time) to the circuit and it does not depend on any other elements or quantity in the circuit.

Direct or Time Invariant Voltage Source

- The voltage source which can produce or deliver constant voltage as output is termed as direct voltage source.
- The flow of electrons will be in one direction that is polarity will be always same.
- The movement of electrons or current will be in one direction always. The value of voltage will not alter with time.
- Example: **DC Generator, Battery Cells**, etc.


Voltage Source

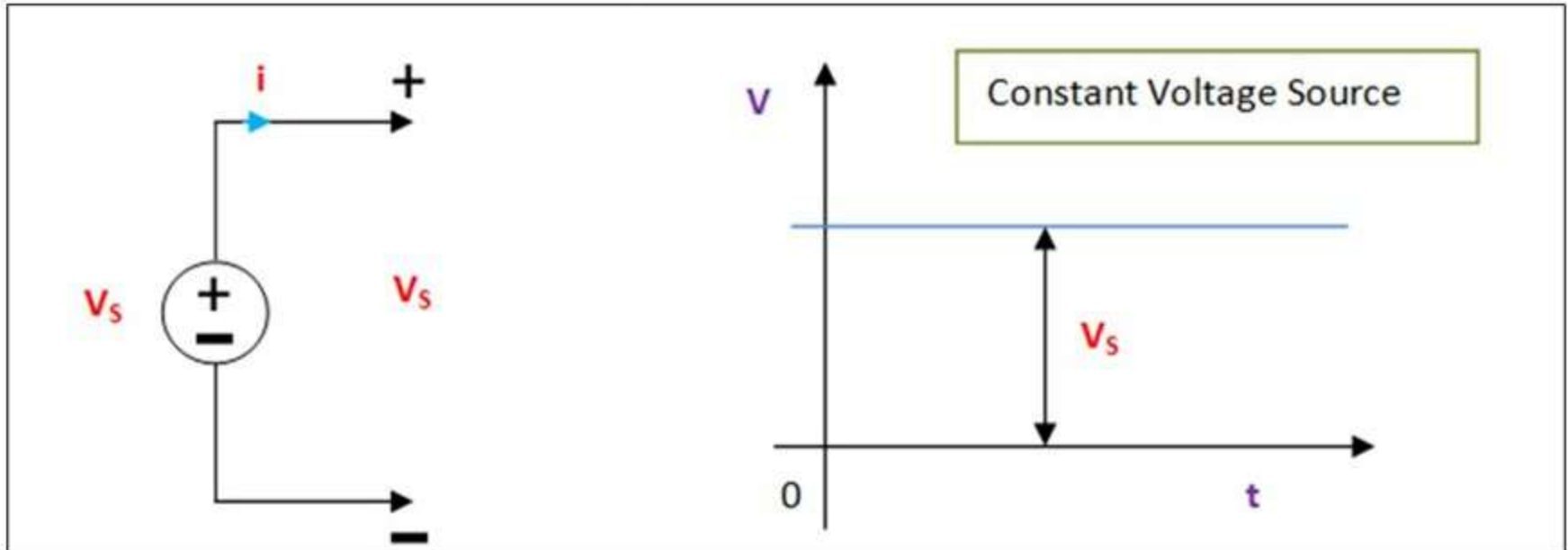

Voltage Source

Alternating Voltage Source

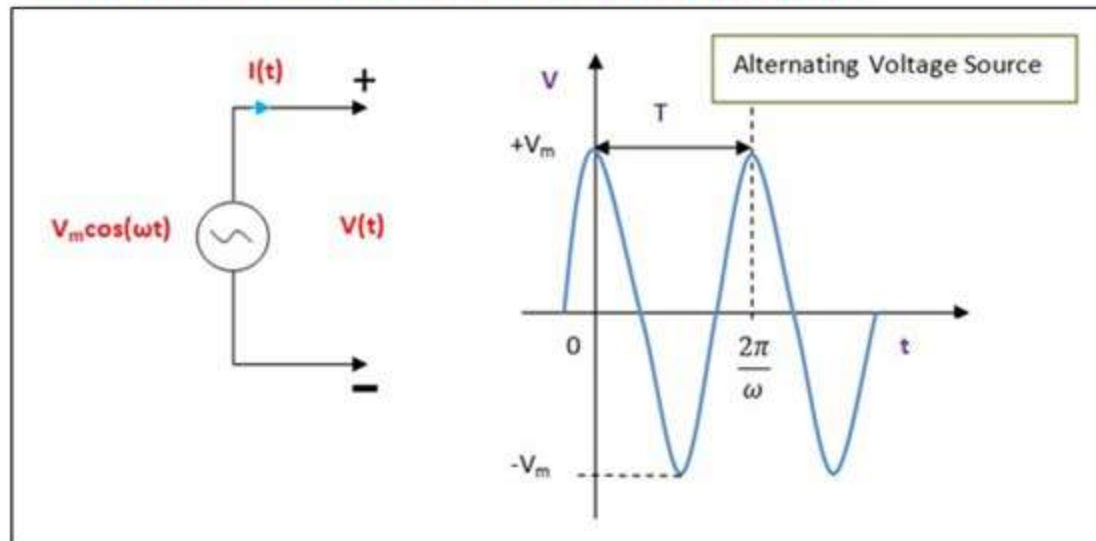- The voltage source which can produce or deliver alternating voltage as output is termed as alternating voltage source.
- Here, the polarity gets reversed at regular intervals.
- This voltage causes the current to flow in a direction for a time and after that in a different direction for another time.
- That means it is time varying.
- Example: **DC to AC converter, Alternator**, etc.




Voltage Source

Dependent Voltage Source

- The voltage source delivers an output voltage which is **not steady or fixed** and it always **depends on other quantities** such as voltage or current in any other part of the circuit.


Voltage Controlled Voltage Source (VCVS)

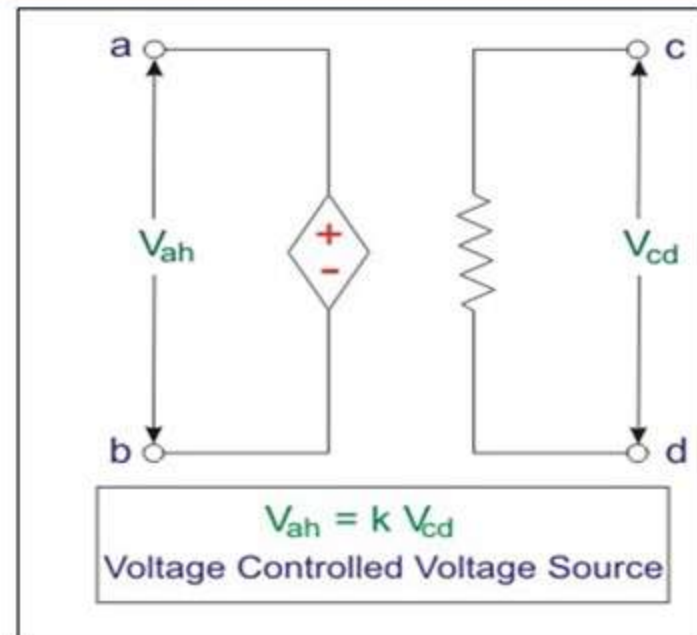- When the voltage source depends on voltage in any other part of the circuit, then it is called **Voltage Controlled Voltage Source (VCVS)**.



Current Controlled Voltage Source (CCVS)

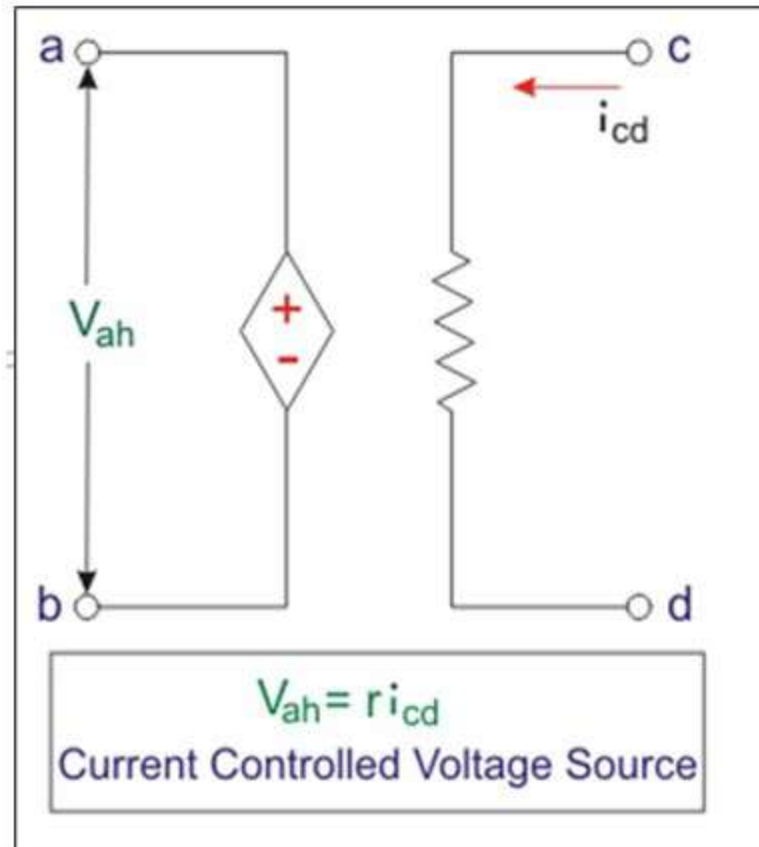
- When the voltage source depends on current in any other part of the circuit, then it is called **Current Controlled Voltage Source (CCVS)**.



Voltage Source

Ideal Voltage Source

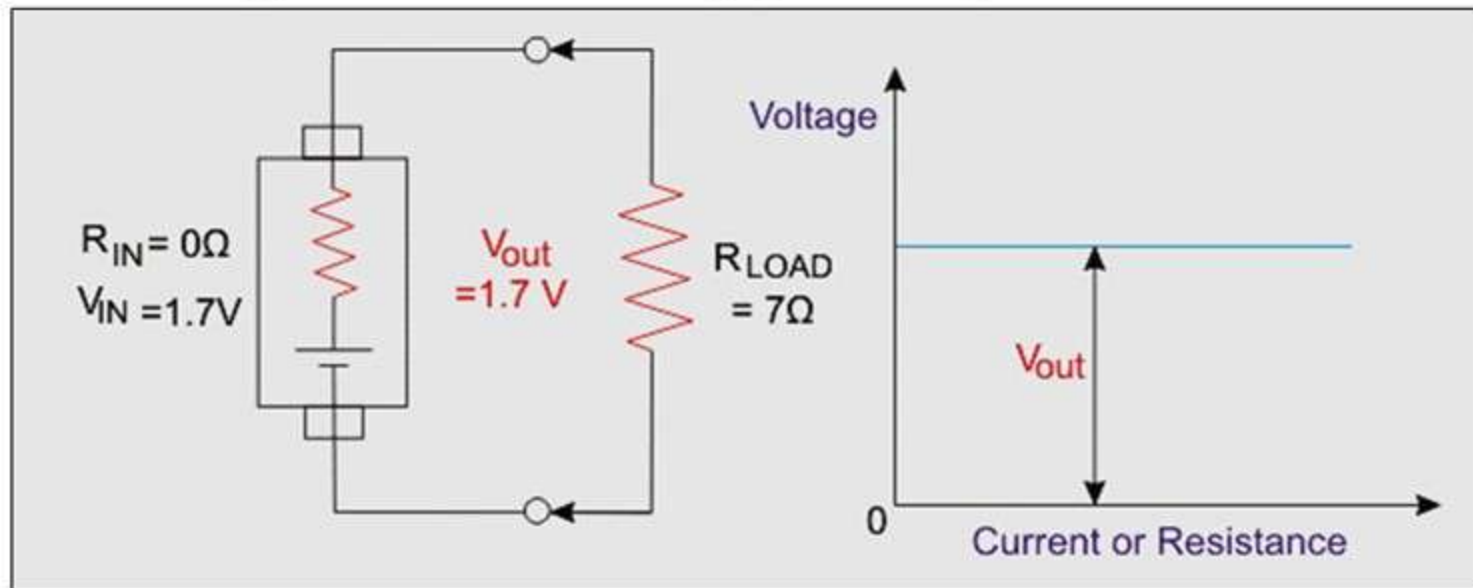
- The voltage source which can deliver **constant voltage** to the circuit which is independent of the current that the circuit draws.
- The value of **internal resistance is zero** so no power is wasted owing to internal resistance.
- It performs as a **100% efficient** voltage source. All of its voltage of the ideal voltage source can drop perfectly to the load.



Voltage Source

Practical Voltage Source

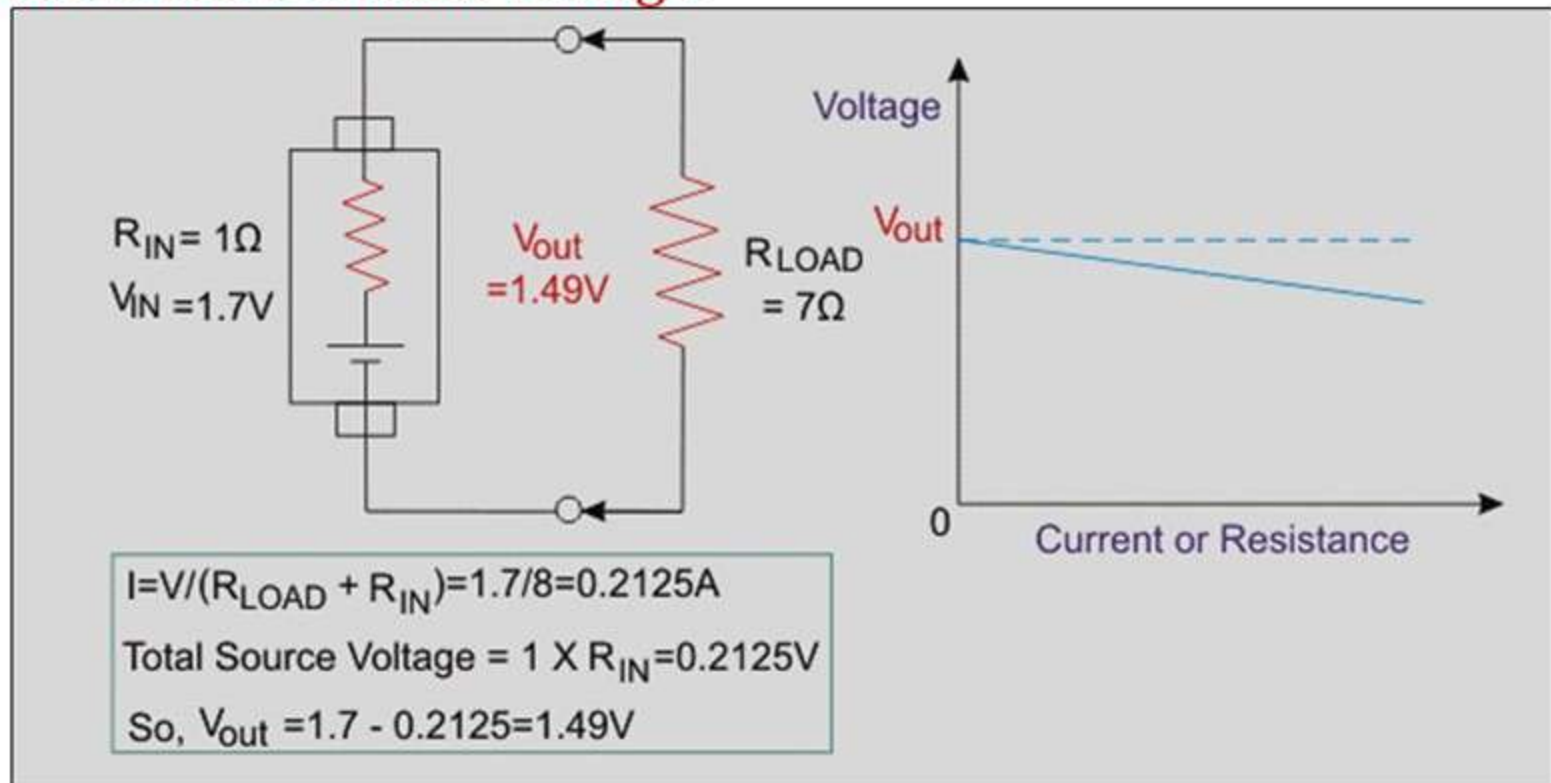- The voltage source having **internal resistance** is known as practical or real voltage source.
- Due to this internal resistance, **voltage drop takes place** which **reduces the terminal voltage**.



Current Source



- A current source is a circuit element that **maintains a constant current flow** regardless of the voltage developed across its terminals as this voltage is determined by other circuit elements.

- 1) Ideal Current Source
- 2) Practical Current Source

Ideal Current Source


- An **ideal current source** is a two-terminal circuit element which supplies the same current to any load resistance connected across its terminals.
- It is important to keep in mind that the current supplied by the current source is independent of the voltage of source terminals.
- It has infinite resistance.

Current Source

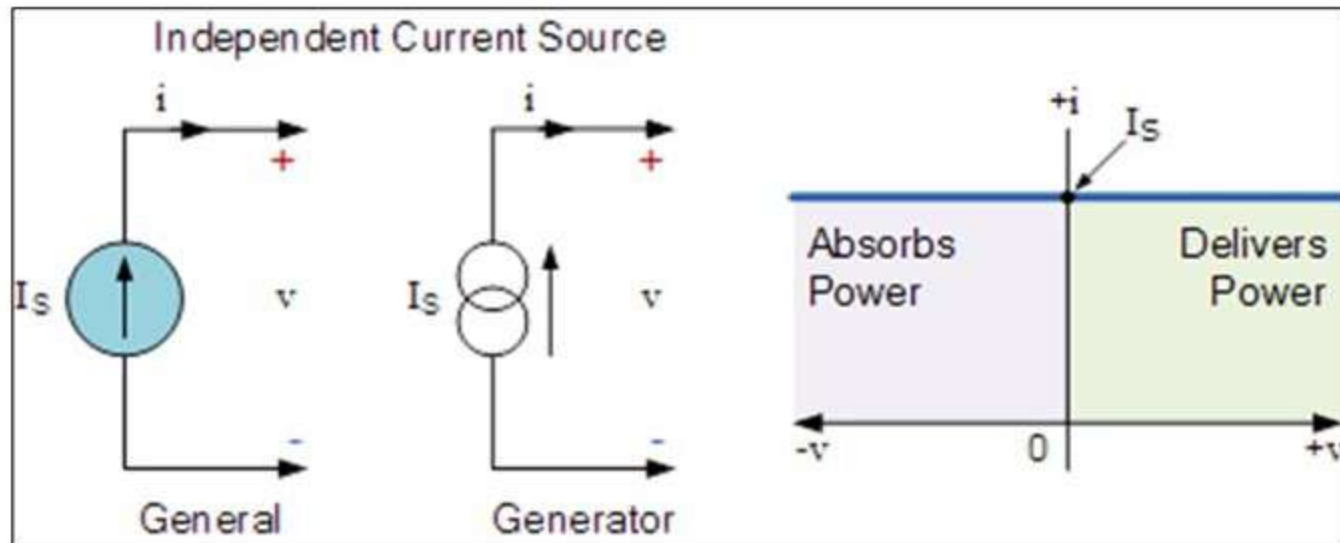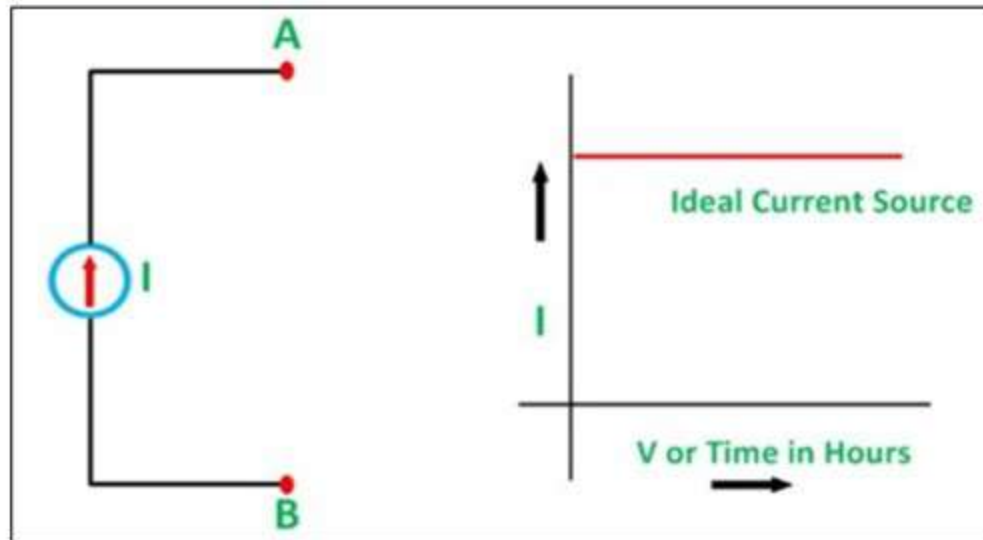

Practical Current Source

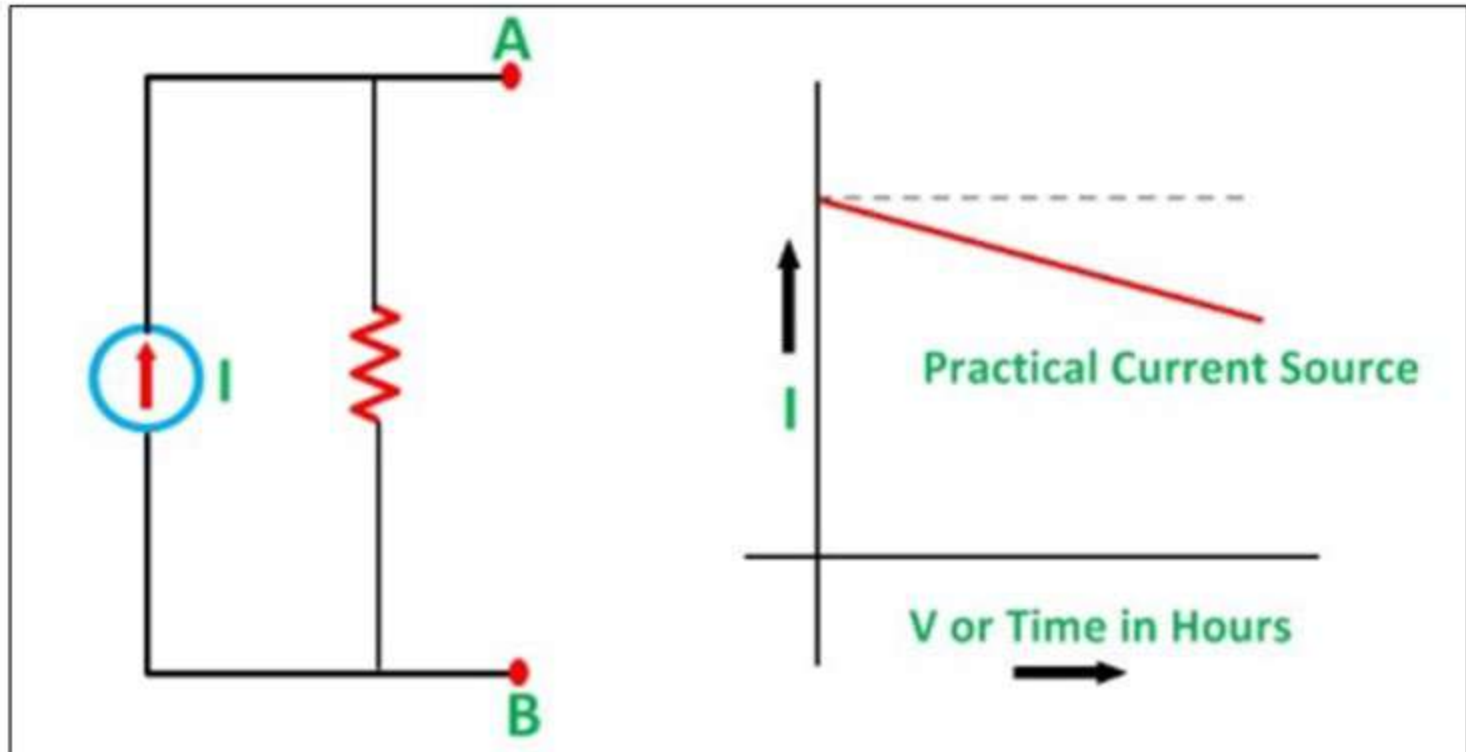- A **practical current source** is represented as an ideal current source connected with the resistance in parallel. The symbolic representation is shown below:




Source Transformation

- **Source Transformation** simply means replacing one source by an equivalent source.
- A practical voltage source can be **transformed** into an **equivalent practical current source** and similarly a practical current source into voltage source.
- Any **practical voltage source** consists of an ideal voltage source in series with an internal resistance or impedance (for an ideal source this impedance will be zero), the output voltage becomes independent of the load current.
- For any **practical current source** or simply current source, there is an ideal current source in parallel with the internal resistance or impedance, for ideal current source this parallel impedance is infinity.
- The voltage and current source are **mutually transferable**.

Source Transformation

➤ Consider a circuit given below:

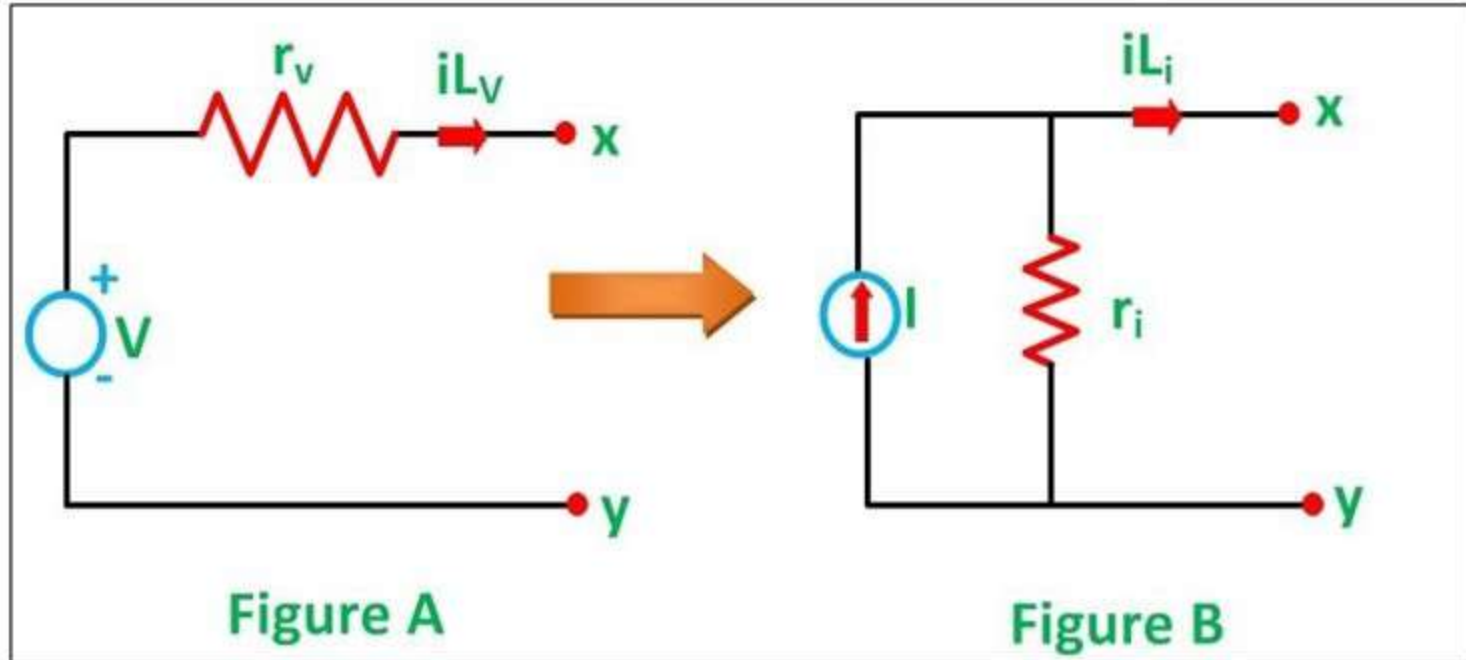

➤ Figure A represents a **practical voltage source** in series with the internal resistance r_v , while figure B represents a **practical current source** with parallel internal resistance r_i .

- For the practical voltage source the load current will be given by the equation:

$$i_{L_v} = \frac{V}{r_v + r_L} \dots \dots \dots (1)$$

Where,

i_{L_v} is the load current for the practical voltage source

V is the voltage

r_v is the internal resistance of the voltage source

r_L is the load resistance

- It is assumed that the load resistance r_L is connected at the terminals x - y .

Source Transformation

- For the practical current source, the load current is given as:

$$iL_i = I \frac{r_i}{r_i + r_L} \dots \dots \dots (2)$$

Where,

iL_i is the load current for the practical current source is the current

r_i is the internal resistance of the current source

r_L is the load resistance connected across the terminal x-y

- Two sources become identical, when we will equate equation (1) and equation (2)

$$\frac{V}{r_v + r_L} = I \frac{r_i}{r_i + r_L}$$

Source Transformation

- However, for the current source, the terminal voltage at x-y would be $I r_i$, x-y terminal are open. i.e.

$$V = I \times r$$


- Therefore

$$\begin{aligned} r_v + r_L &= r_i + r_L \\ r_v &= r_i \end{aligned}$$

- Therefore, for any practical voltage source, if the ideal voltage is V and internal resistance be r_v , the voltage source can be replaced by a current source I with the internal resistance in parallel with the current source.

Source Transformation

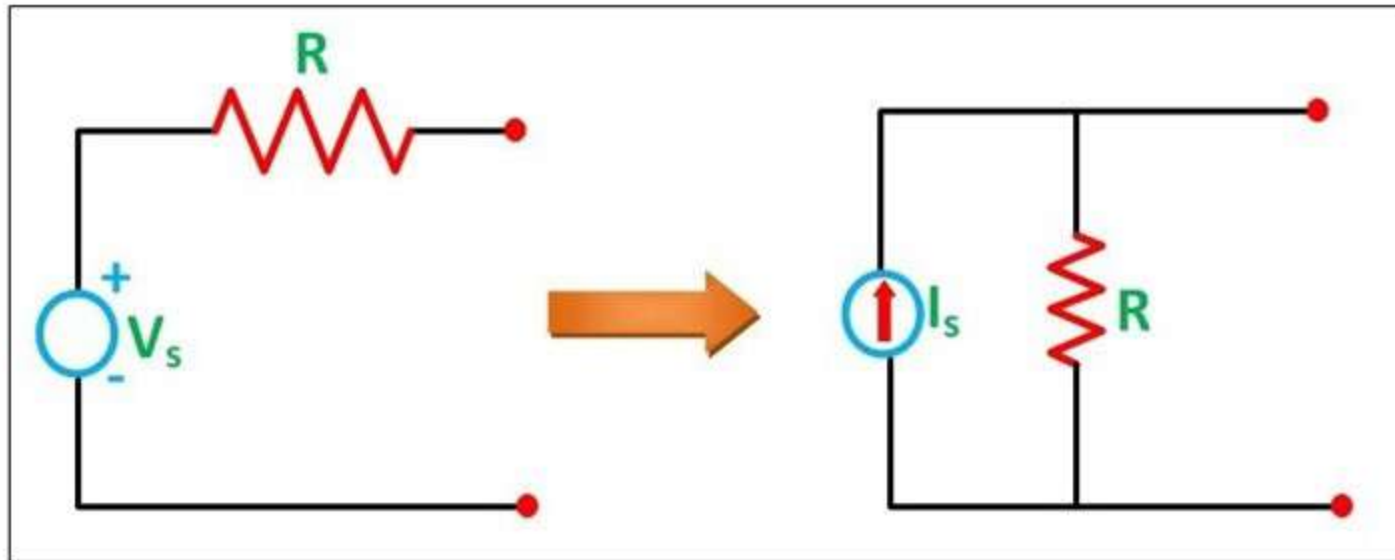Conversion of Voltage Source into Current Source




- When the voltage source is connected with the resistance in series and it has to be converted into the current source then the resistance is connected in parallel with the current source as shown in the above figure.

- Where

$$I_s = V_s / R$$

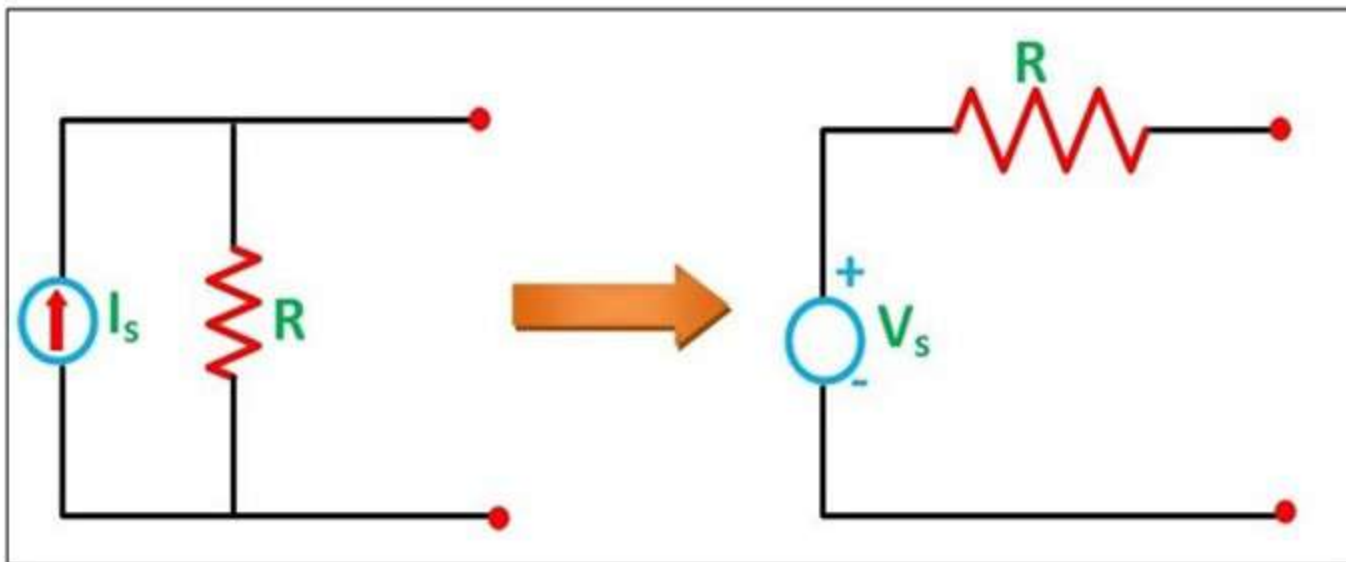Conversion of Current Source into Voltage Source



- In the above circuit diagram a current source which is connected in parallel with the resistance is transformed into a voltage source by placing the resistance in series with the voltage source.


- Where

$$V_s = I_s R$$

What are Kirchhoff's Laws?

- **Kirchhoff's laws** govern the conservation of charge and energy in electrical circuits.
- Kirchhoff's circuit laws allow us to solve complex circuit problems by defining a set of basic network laws and theorems for the voltages and currents around a circuit.

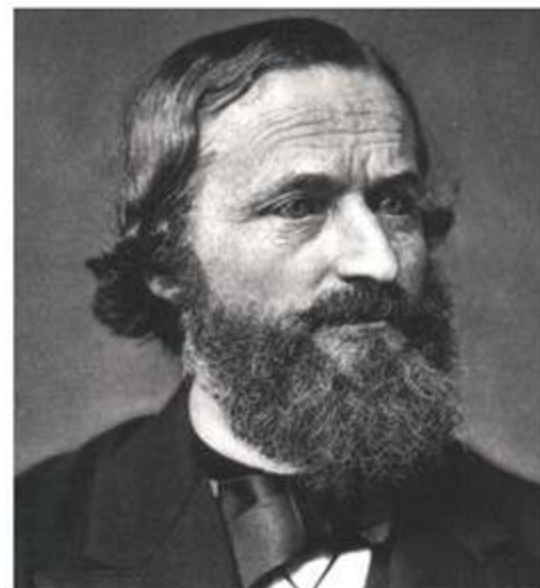- 1) Kirchhoff's Current Law (KCL)
- 2) Kirchhoff's Voltage Law (KVL).



Gustav Kirchhoff

Kirchhoff's Current Law (KCL)

At any node (junction) in an electrical circuit, the sum of currents flowing into that node is equal to the sum of currents flowing out of that node.

OR


The algebraic sum of currents in a network of conductors meeting at a point is zero.

$$\sum I_{in} = \sum I_{out}$$

- The sum of currents entering the junction are thus equal to the sum of currents leaving.
- This implies that the current is **conserved** (no loss of current).

Kirchhoff's Laws

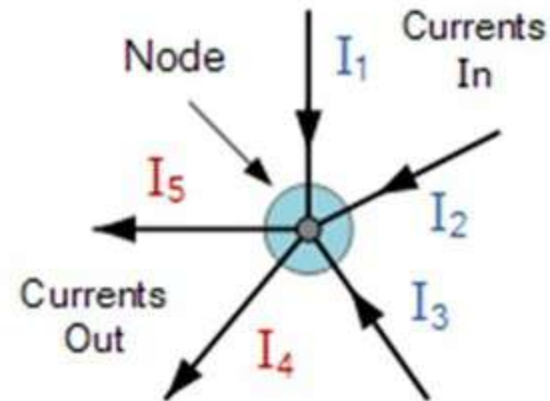Currents Entering the Node
Equals
Currents Leaving the Node



$$I_1 + I_2 + I_3 + (-I_4 + -I_5) = 0$$

- Current entering the node is considered positive and leaving the node is considered negative in value.

$$I_1 + I_2 + I_3 - I_4 - I_5 = 0$$

$$\therefore I_1 + I_2 + I_3 = I_4 + I_5$$

Kirchhoff's Voltage Law (KVL)

In any closed loop network, the total voltage around the loop is equal to the sum of all the voltage drops within the same loop.

OR

In other words the algebraic sum of all voltages within the loop must be equal to zero.

$$\sum V - \sum (I \times R) = 0$$

$$\therefore \sum \Delta V_{\text{closed loop}} = 0$$

➤ This idea by Kirchhoff is known as the **Conservation of Energy**.



Kirchhoff's Laws

Sign Conventions for KVL

For emf (Voltage Source)

+V:
Travel direction
from - to +



-V:
Travel direction
from + to -

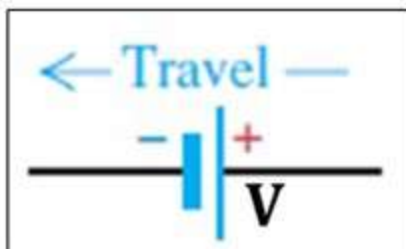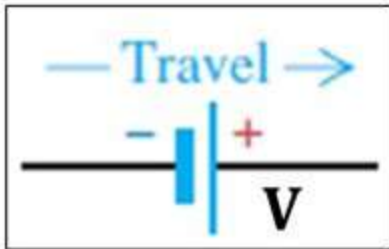

For Voltage Drop in Resistor

+IR:
Travel direction
from - to +


-IR:
Travel direction
from + to -

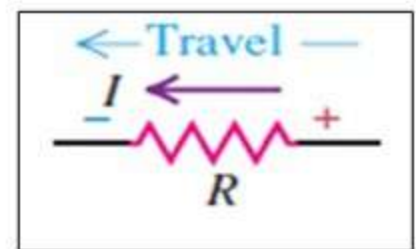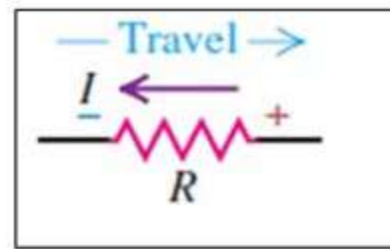

Kirchhoff's Laws

- Consider the closed path **ABCD** in figure. As we travel around the mesh in the clockwise direction, different voltage drops will have the following signs:

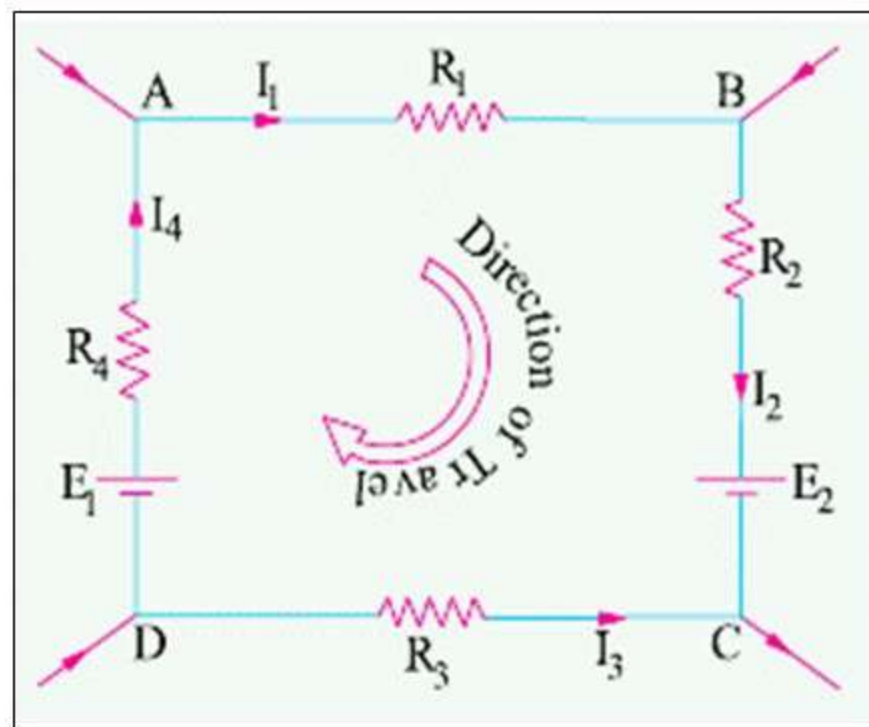
$I_1 R_1$ is -ve (fall in potential)
 $I_2 R_2$ is -ve (fall in potential)
 $I_3 R_3$ is +ve (rise in potential)
 $I_4 R_4$ is -ve (fall in potential)
 E_2 is -ve (fall in potential)
 E_1 is +ve (rise in potential)



$$-I_1 R_1 - I_2 R_2 + I_3 R_3 - I_4 R_4 - E_2 + E_1 = 0$$


$$I_3 R_3 + E_1 = I_1 R_1 + I_2 R_2 + I_4 R_4 + E_2$$

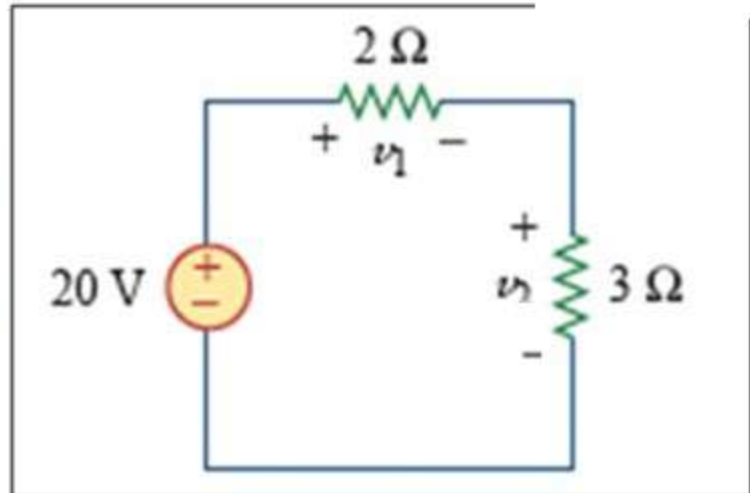Example-1: For the circuit in figure, find voltages v_1 and v_2 .



➤ To find and we apply **Ohm's law** and **Kirchhoff's voltage law**.

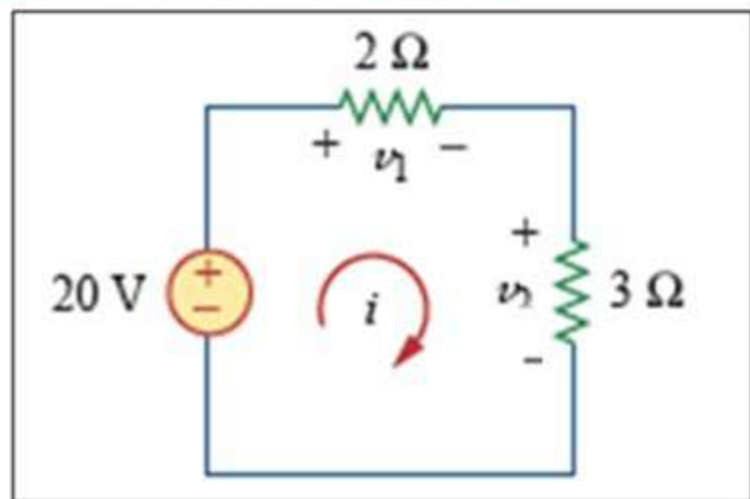➤ Assume that current i flows through the loop as shown in figure.



Kirchhoff's Laws

➤ From ohm's law

➤ $V_1 = 2 \times i$ $V_2 = 3 \times i$ _____ (1)

➤ Applying KVL around the loop gives

➤ $20 - V_1 - V_2 = 0$ _____ (2)


➤ Substituting Eq.(1) into Eq.(2)

➤ $20 - 2i - 3i = 0$ or $5i = 20$ therefore, $i = 4$ A.


➤ Substituting i in Eq.(1) finally gives

➤ $V_1 = 2 \times i = 8$ V and $V_2 = 3 \times i = 12$ V.

Kirchhoff's Laws

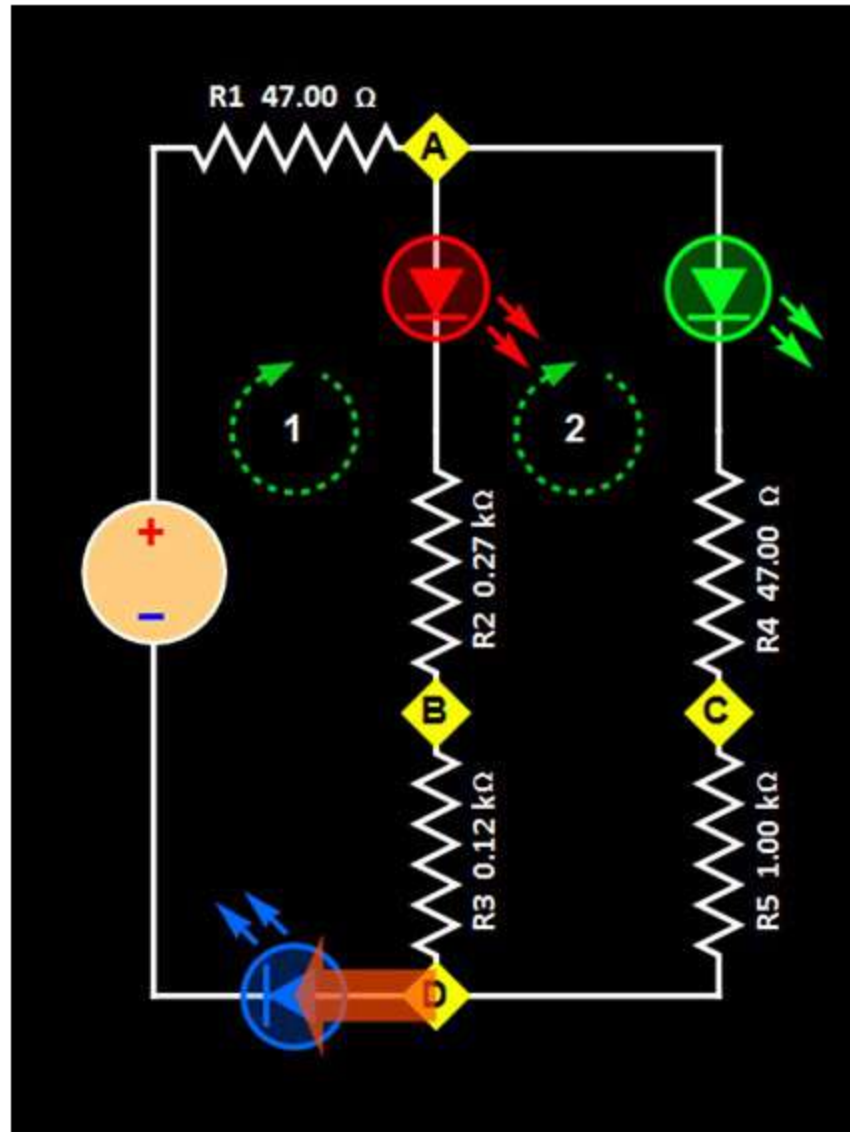

Observations from the Circuit

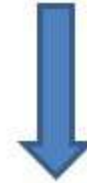

Junction: A & D



Loop: ABDA & ACDBA

Current follows the Ohm's law

$$I \propto \frac{1}{R}$$

Kirchhoff's Laws

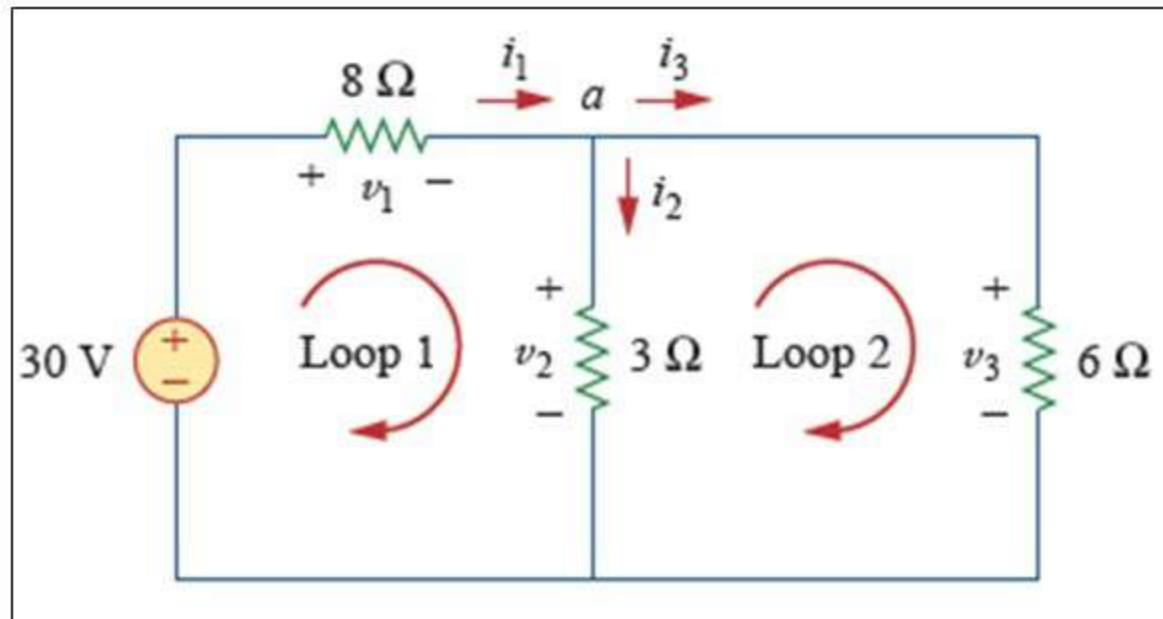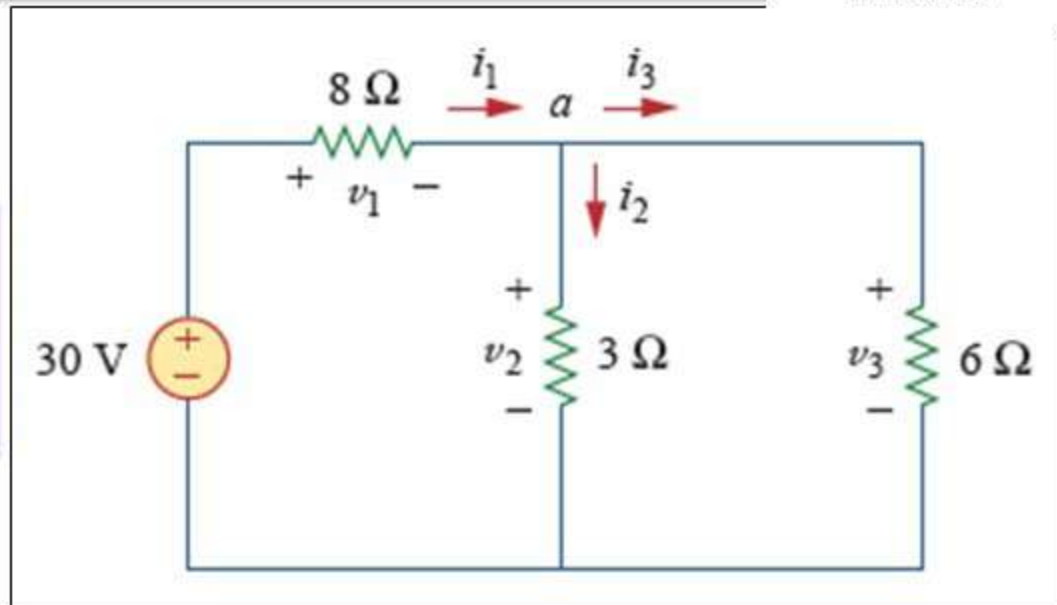Example-2: Find currents and voltages in the circuit shown.



- We will apply Ohm's Law and Kirchhoff's Laws. By Ohm's Law,
- $V_1 = 8 \times I_1$ $V_2 = 3 \times I_2$ $V_3 = 6 \times I_3$
- Applying KCL at node a,
- $i_1 - i_2 - i_3 = 0$ _____ (1)
- Applying KVL to Loop 1,
- $30 - V_1 - V_2 = 0$ _____ (2)
- We express Eq.(2) in terms of i_1 and i_2
- $30 - (8 \times I_1) - (3 \times I_2) = 0$ _____ (3)
- Therefore, $i_1 = [30 - (3 \times I_2)] / 8$

- Applying KVL to Loop 2,
- $-V_3 + V_2 = 0$. Therefore, $V_2 = V_3$
- As expected, since the two resistors are in parallel, we will express two voltage drops V_2 and V_3 in terms of currents i_2 and i_3
- $6 \times I_3 = 3 \times I_2$. Therefore, $I_3 = I_2 / 2$
- Now putting the values of i_1 , i_2 and i_3 in Eq.(1) we get,
- $[30 - (3 \times I_2)] / 8 - i_2 - I_2 / 2 = 0$
- $30 - 3 I_2 - 8 i_2 - 4 i_2 = 0$

Kirchhoff's Laws

- $30 - 3 I_2 - 8 i_2 - 4 i_2 = 0$
- $30 - 15 I_2 = 0$
- Which gives the value of $I_2 = 2 \text{ A}$.
- From the value of I_2 the value of $i_1 = [30 - (3 \times I_2)] / 8 = 3 \text{ A}$
and $I_3 = I_2 / 2 = 1 \text{ A}$.
- $V_1 = 8 \times I_1 = 24 \text{ V}$,
- $V_2 = 3 \times I_2 = 6 \text{ V}$,
- $V_3 = 6 \times I_3 = 6 \text{ V}$.

Star-Delta Transformation

- Standard 3-phase circuits or networks take on two major forms with names that represent **the way in which the resistances are connected**

- 1) a **Star** connected network which has the symbol of the letter, **Y (wye)**
- 2) a **Delta** connected network which has the symbol of a triangle, **Δ /D (delta)**


- If a 3-phase, 3-wire supply or a 3-phase load is connected in one type of configuration, it can be easily transformed or changed it into an equivalent configuration of the other type by using

- 1) Star-Delta Transformation
- 2) Delta-Star Transformation

Star-Delta Transformation

Star Connection

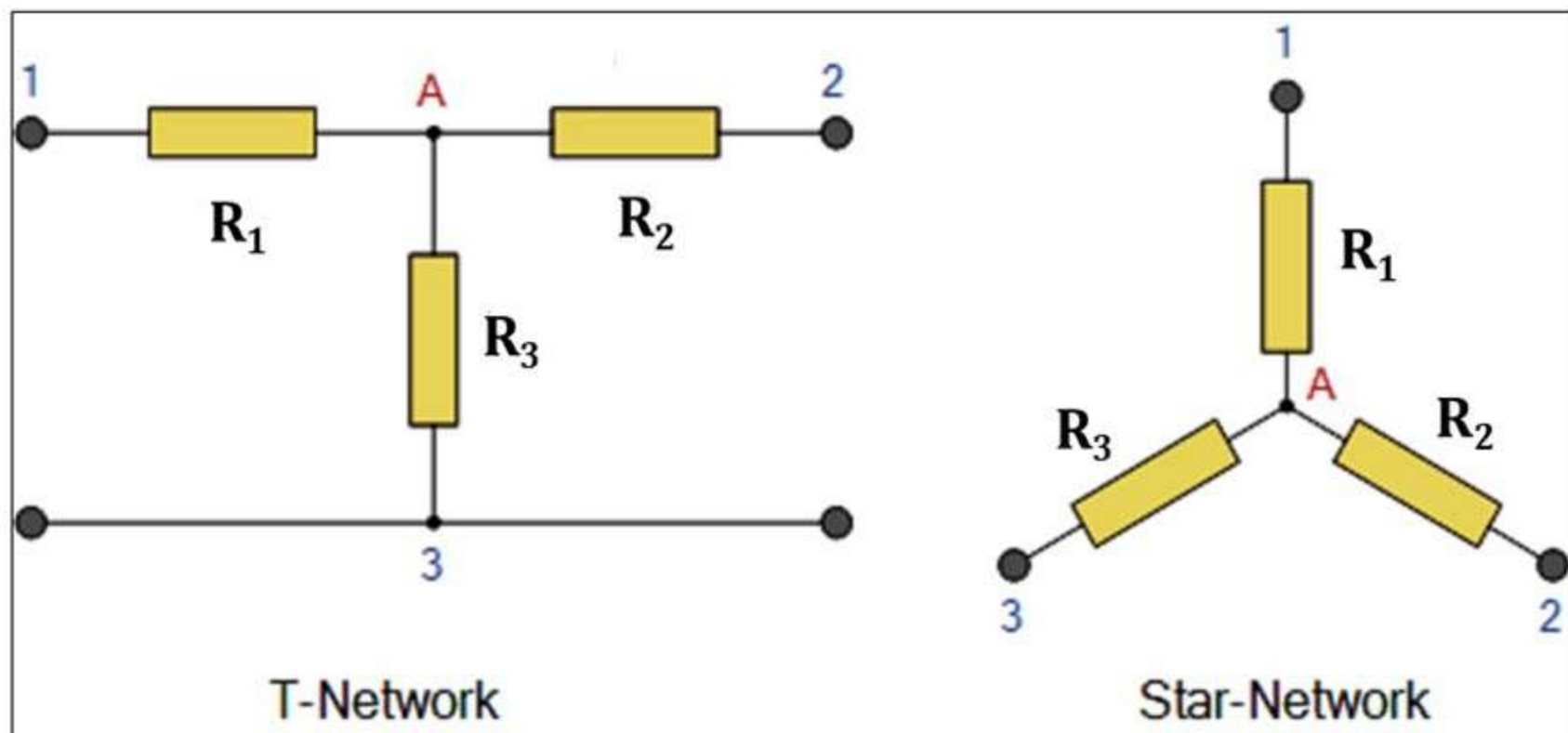
- A resistive network consisting of three resistors can be connected together to form a **T** or “**Tee**” configuration but the network can also be redrawn to form a **Star** or **Y** type network as shown below.



Star-Delta Transformation


Delta Connection

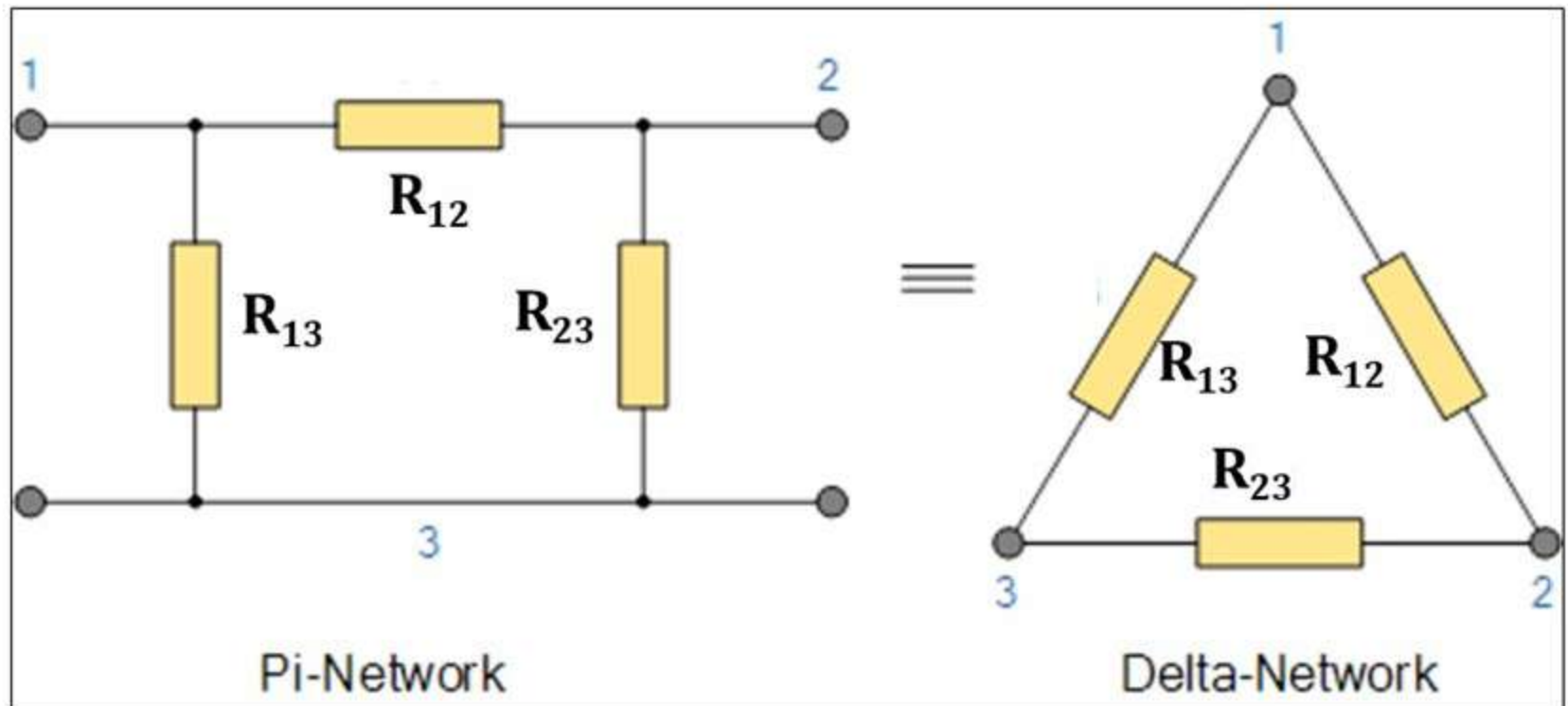- A resistive network consisting of three resistors can be connected together to form a π or “Pi” configuration but the network can also be redrawn to form a **Delta** or Δ/D type network as shown below.



Star-Delta Transformation

Delta to Equivalent Star Network

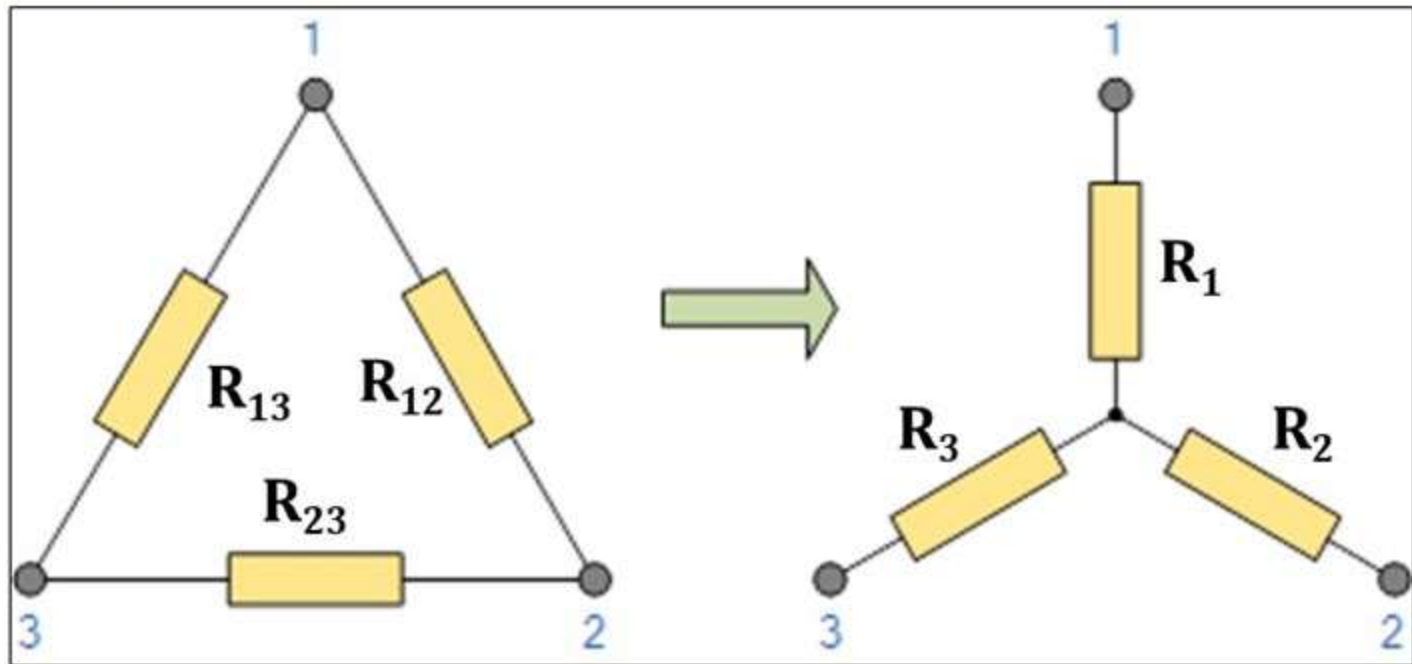

- Compare the resistances between terminals **1 and 2**.

$$R_1 + R_2 = R_{12} \parallel (R_{23} + R_{31})$$

$$\therefore R_1 + R_2 = \frac{R_{12}(R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})} \quad (1)$$

Star-Delta Transformation

- Resistance between the terminals **2 and 3**.

$$\begin{aligned} R_2 + R_3 &= R_{23} \parallel (R_{31} + R_{12}) \\ \therefore R_2 + R_3 &= \frac{R_{23}(R_{31} + R_{12})}{(R_{12} + R_{23} + R_{31})} \quad (2) \end{aligned}$$

- Resistance between the terminals **1 and 3**.

$$\begin{aligned} R_3 + R_1 &= R_{31} \parallel (R_{12} + R_{23}) \\ \therefore R_3 + R_1 &= \frac{R_{31}(R_{12} + R_{23})}{(R_{12} + R_{23} + R_{31})} \quad (3) \end{aligned}$$

Star-Delta Transformation

- Subtracting Eq. (2) from Eq. (1) and adding the result to Eq. (3), we have,

$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} \quad (4)$$


- Similarly, we get,

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} \quad (5)$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} \quad (6)$$

Star-Delta Transformation

Star to Equivalent Delta Network

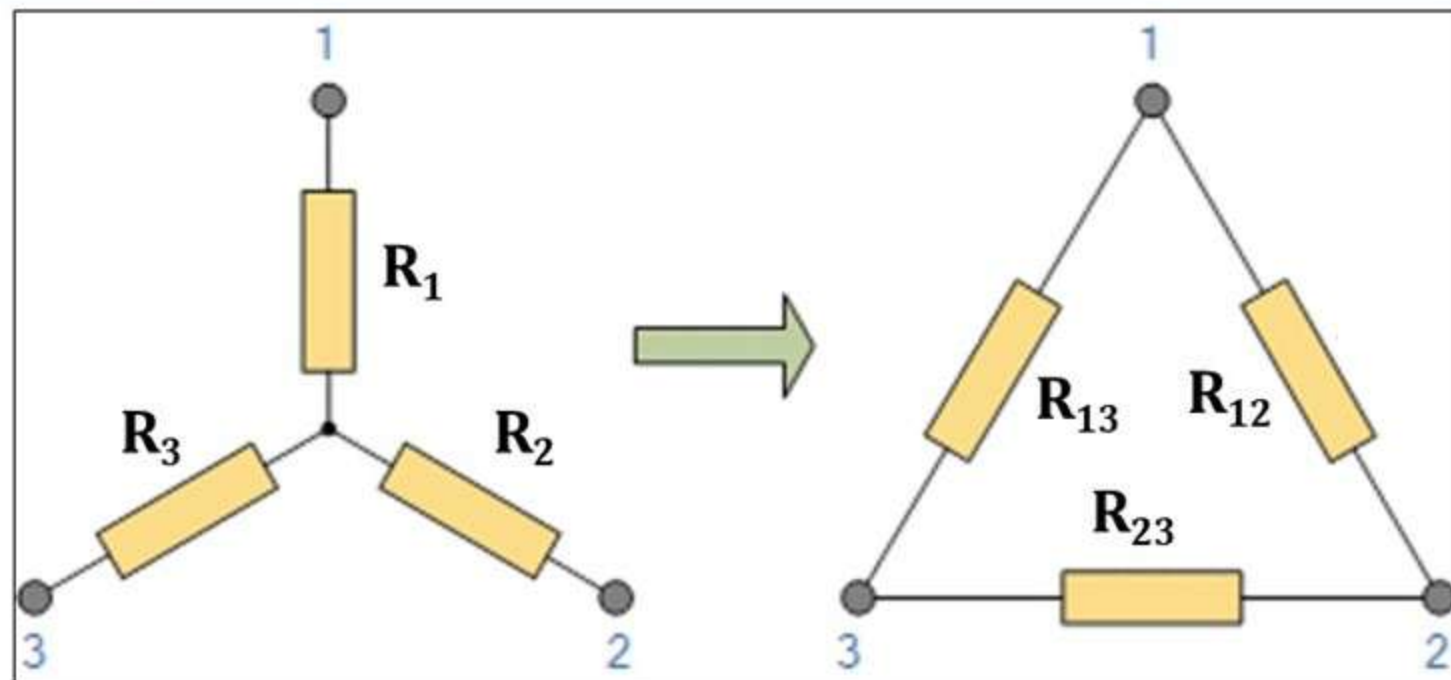

➤ Dividing Eq. (4) by (5), we have,

$$\frac{R_1}{R_2} = \frac{R_{31}}{R_{23}}$$

$$\therefore R_{31} = \frac{R_1 R_{23}}{R_2}$$

Star-Delta Transformation

- Dividing Eq. (4) by (6), we have,

$$\frac{R_1}{R_3} = \frac{R_{12}}{R_{23}}$$
$$\therefore R_{12} = \frac{R_1 R_{23}}{R_3}$$

- Substituting the values of **R_{31}** and **R_{12}** in **Eq. (4)**, we have,


$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

- Similarly,



$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Star-Delta Transformation


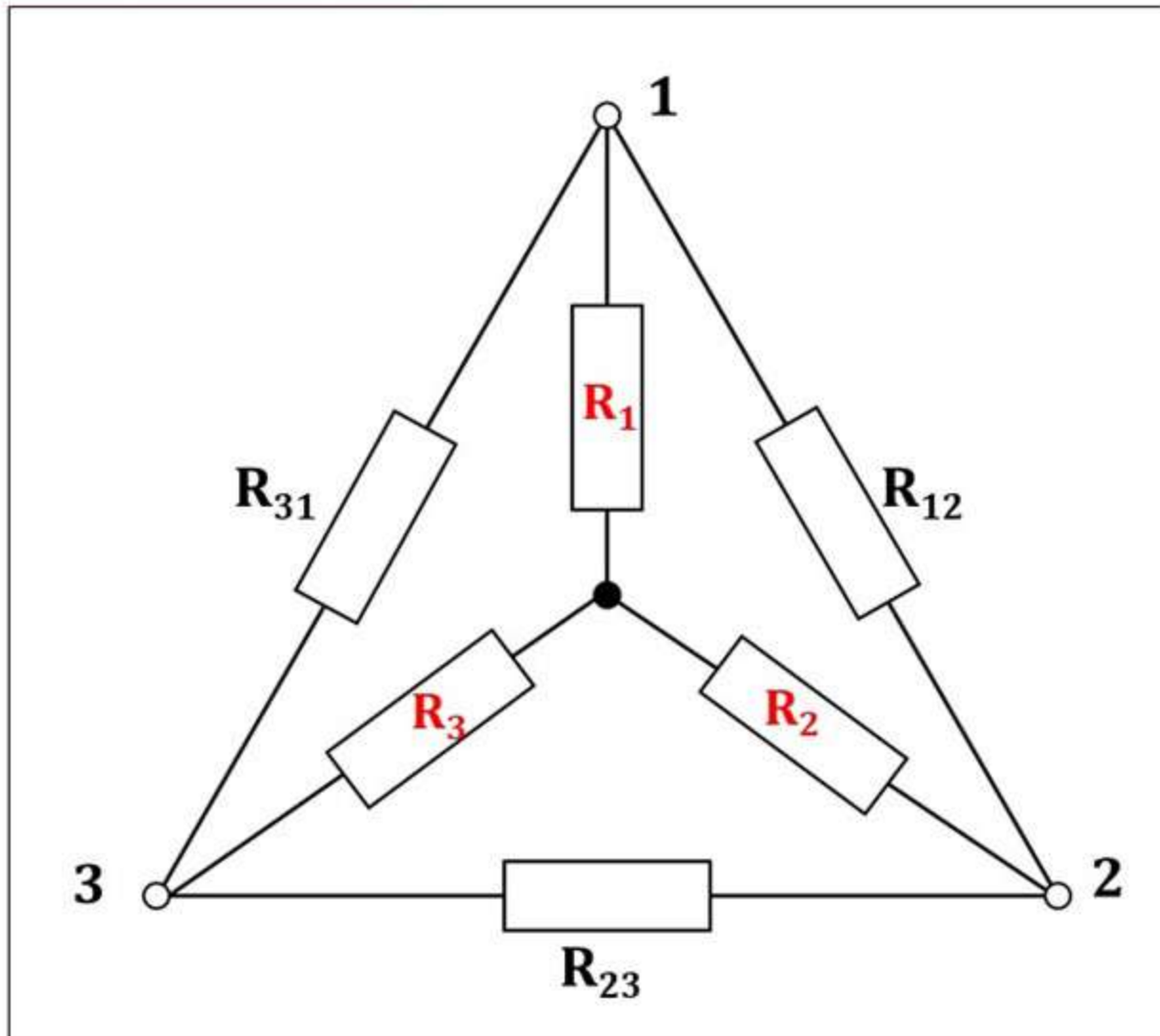


Electromagnetism

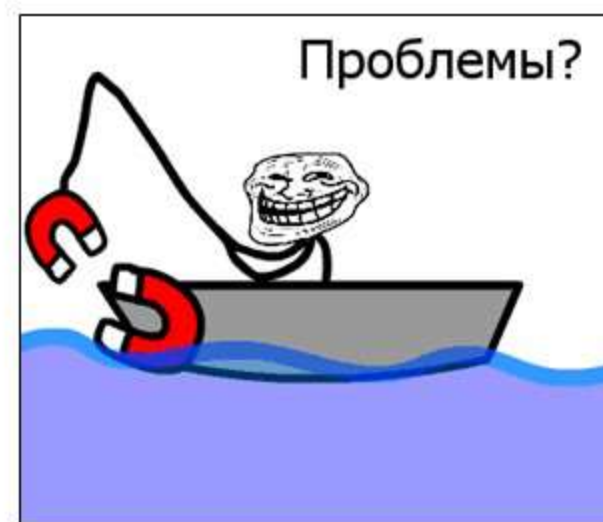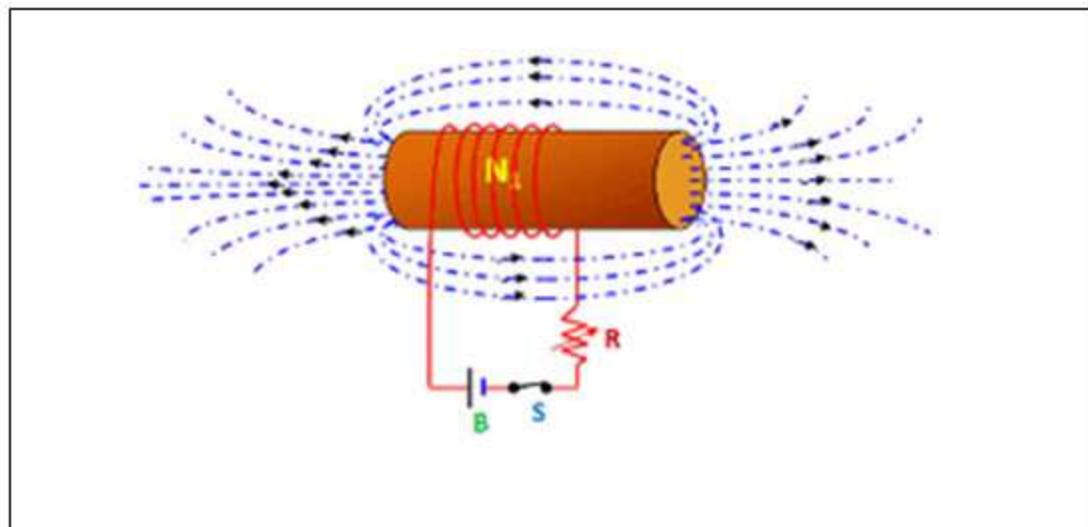



Magnetic Field

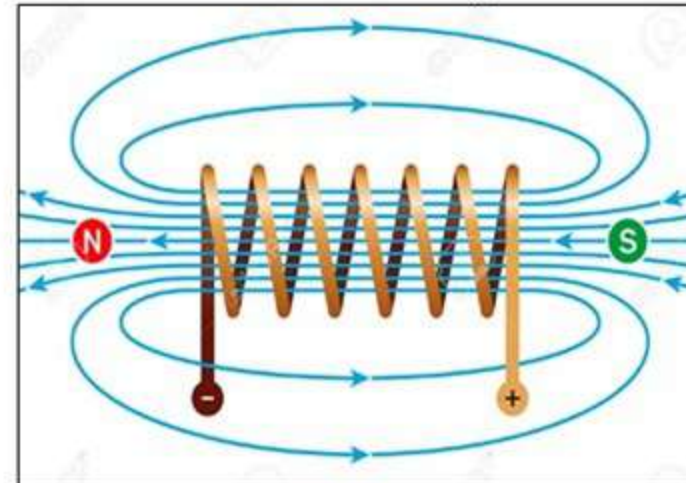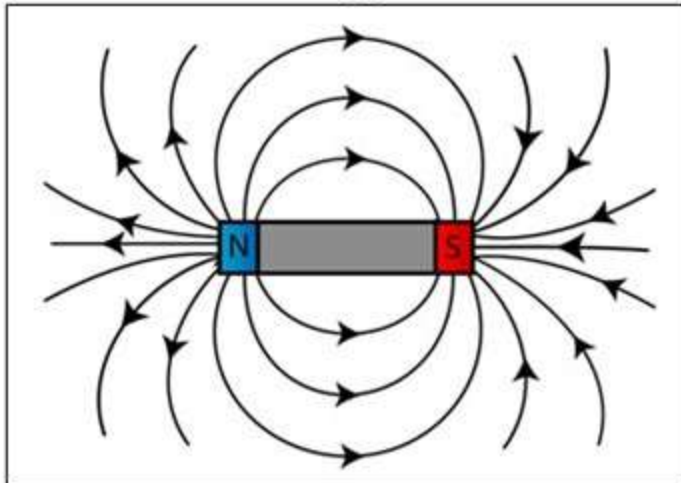- **Magnetic field** is a force generated due to energy change in a volume of space.
- A **magnetic field** is produced by an **electrical charge in motion** e.g. current flowing in a conductor, orbital movement and spin of electrons.
- The magnetic field can be described by **imaginary lines** as shown in the figure for a magnet and a current loop.



Magnetic Field: Permanent Magnet

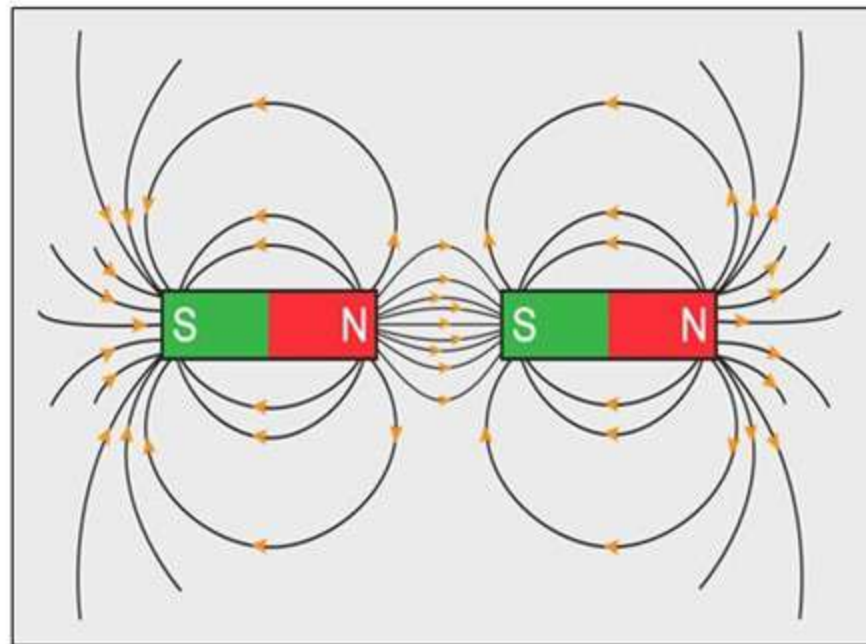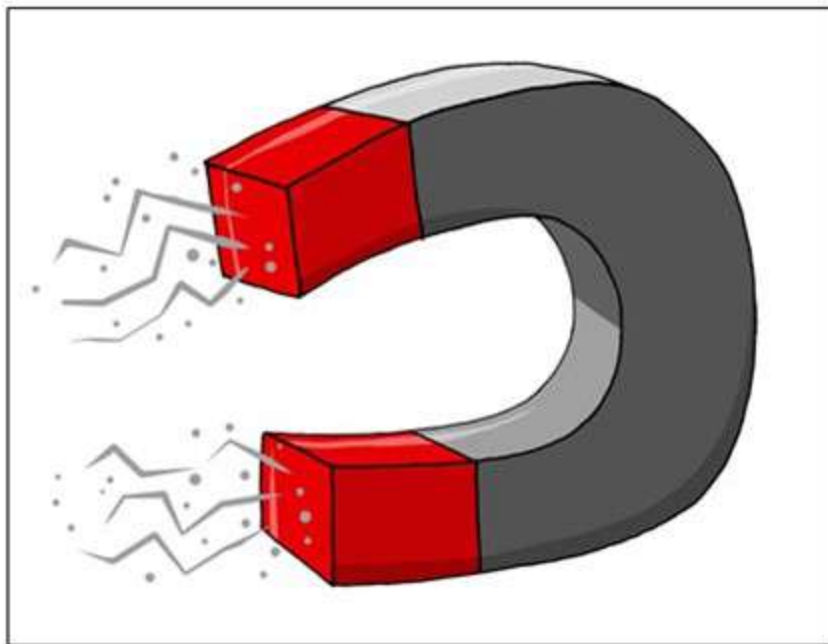➤ There are the orbital motions and spins of electrons within the **permanent magnet** material which lead to a **magnetization** within the material and a magnetic field outside.





Magnetic field of permanent magnet cannot be changed.

Electromagnetism

Magnetic Field: Electromagnet

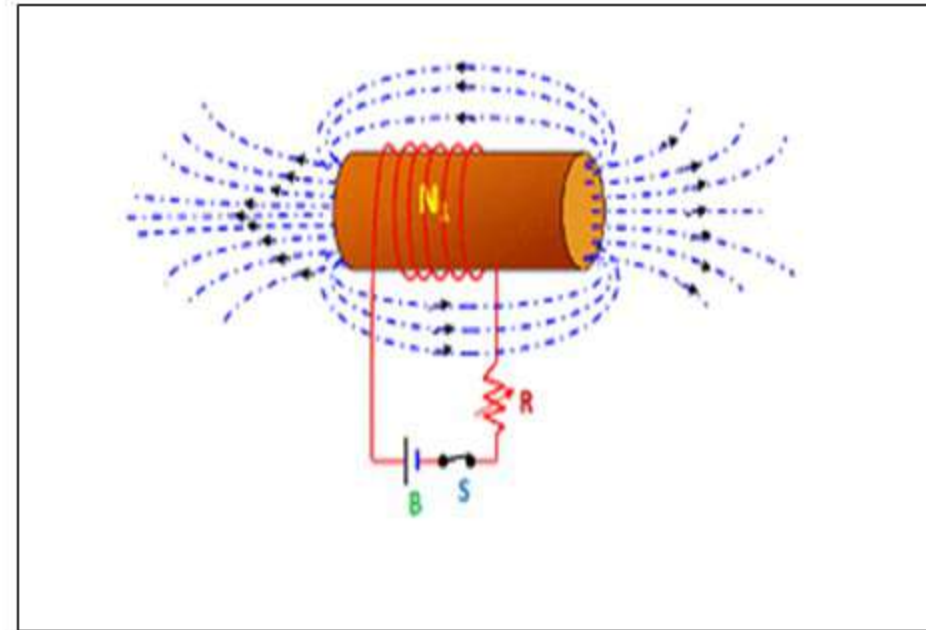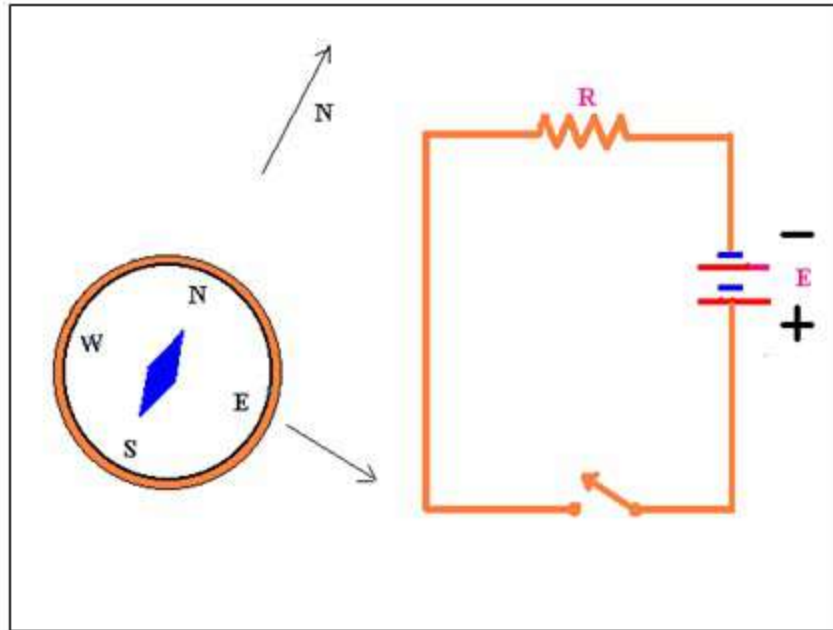➤ Here, Magnetism **exists only when current flows** through the coil/winding placed on a magnetic material.




Controllable magnetic field can be created.



Electromagnetism

Laws of Magnetic Force (Coulomb's Laws)

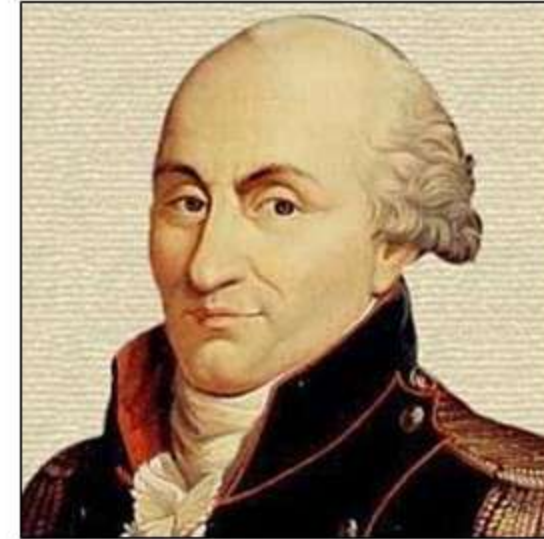- **First Law:** Like poles **repel** each other while unlike poles **attract** each other.




Charles Coulomb

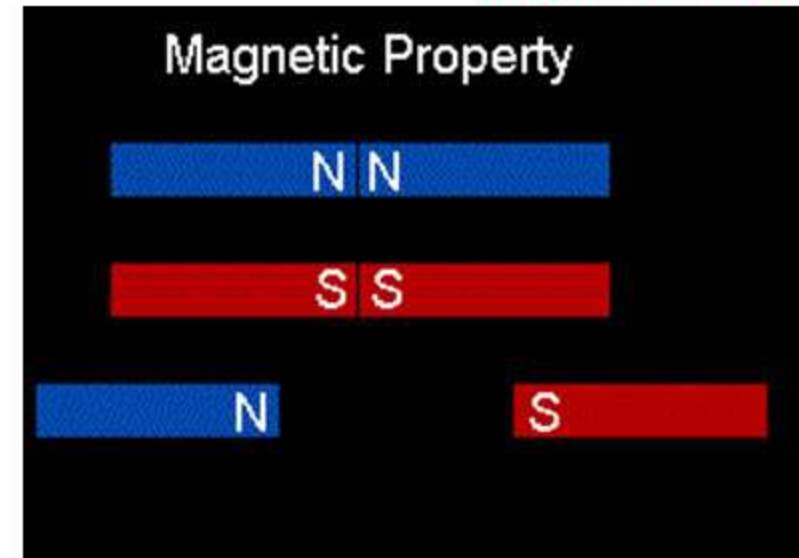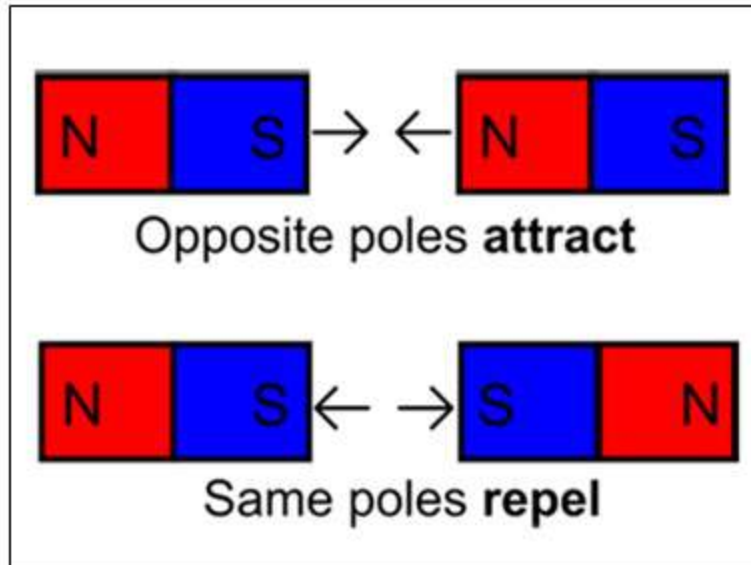

Laws of Magnetic Force (Coulomb's Laws)

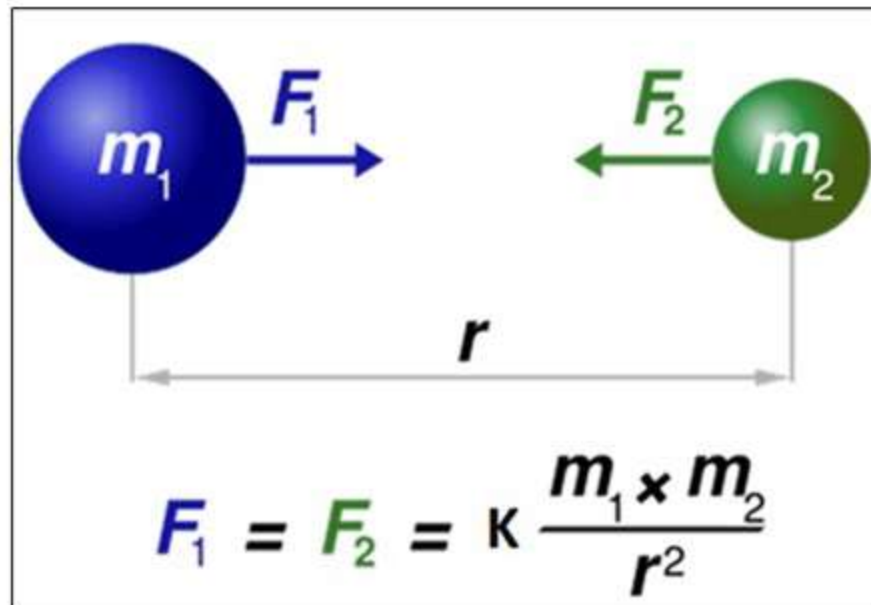- **Second Law:** The force between two magnetic poles is **directly proportional to the product of their pole strengths** and **inversely proportional to the square of distance** between their centers.



$$\text{Where, } K = \frac{1}{4\pi\mu_0\mu_r}$$


μ_0 = Absolute permeability
= $4\pi \times 10^{-7}$ H/m
 μ_r = Relative permeability

Faraday's Law of Electromagnetic Induction

- While **Oersted's** surprising discovery of electromagnetism paved the way for more practical applications of electricity, it was **Michael Faraday** who gave us the key to the practical generation of electricity: **electromagnetic induction**.



Hans Oersted
(1777-1851)

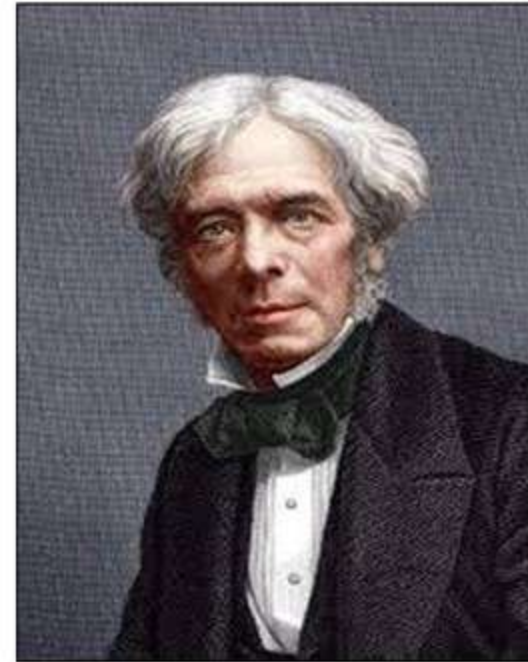


Michael Faraday
(1791-1867)

What Electromagnetic induction?


- Electromagnetic induction is the process by which a current can be induced to flow due to a changing magnetic field.

Faraday's Experiment

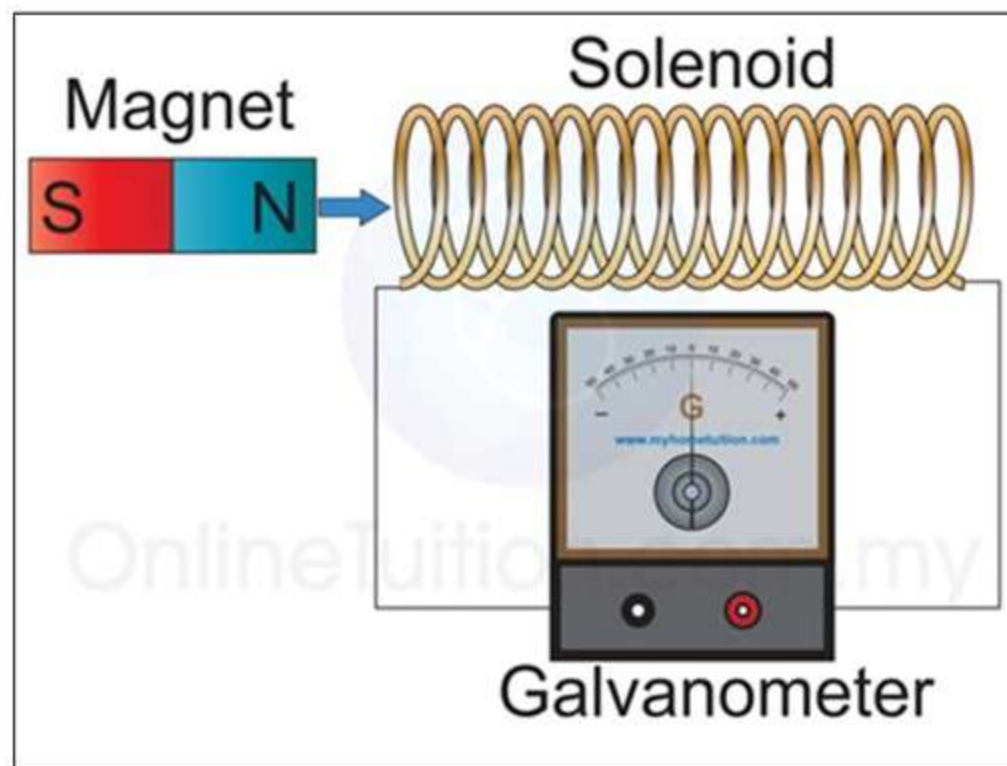

Electromagnetism


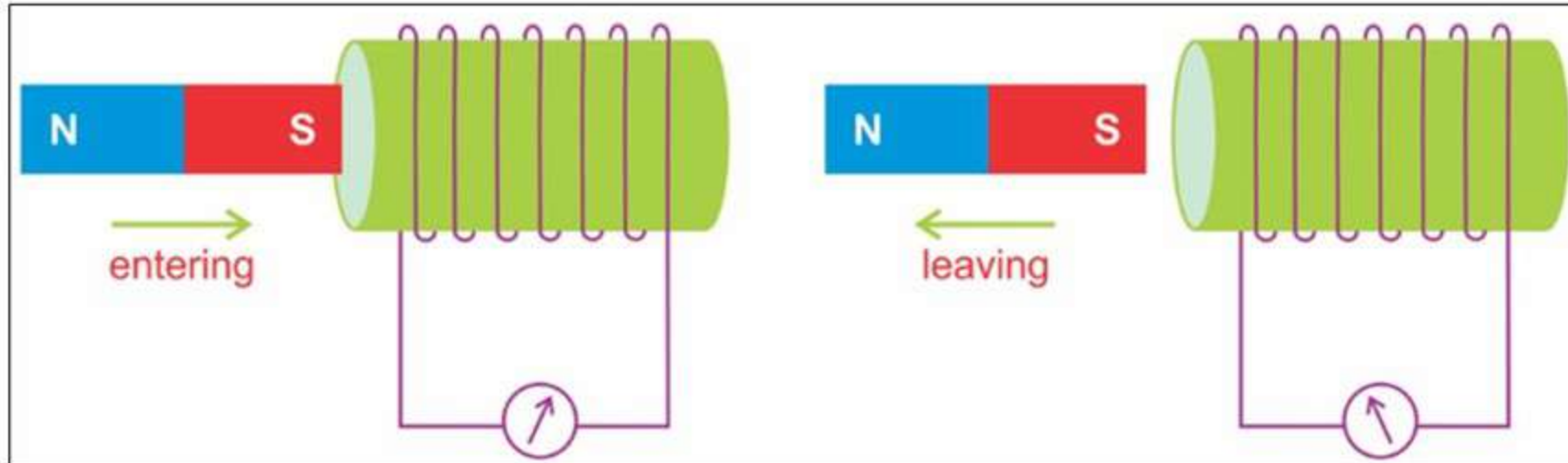
- Faraday discovered that when he moved a magnet near a wire a voltage was generated across the conductor.
- If the magnet was held stationary no voltage was generated, the voltage only existed while the magnet or coil was moving.



- This voltage is known as “**induced emf/voltage**” and the current due to this voltage is called “**induced current**”.

Electromagnetism

Faradays Law of Induction

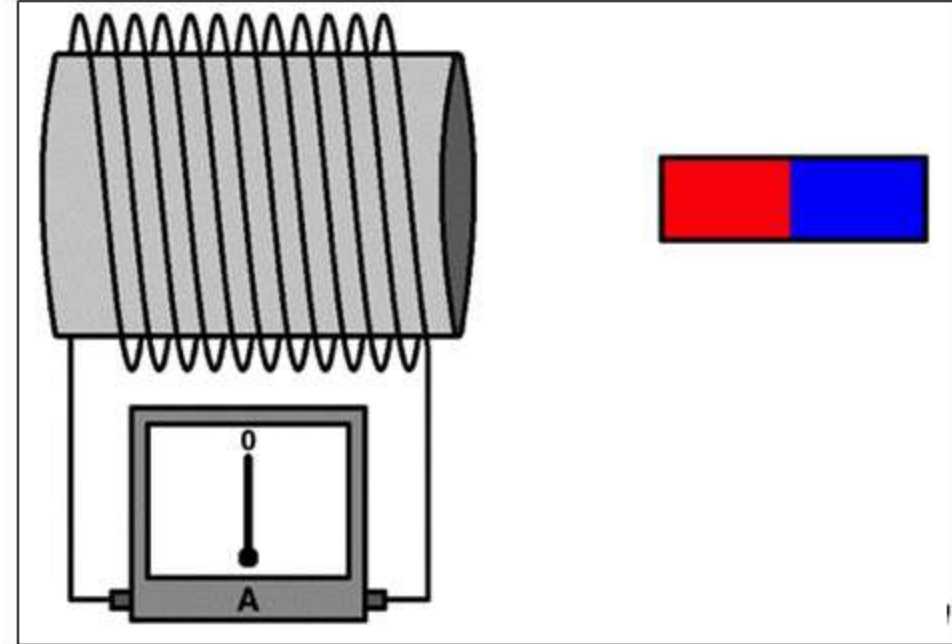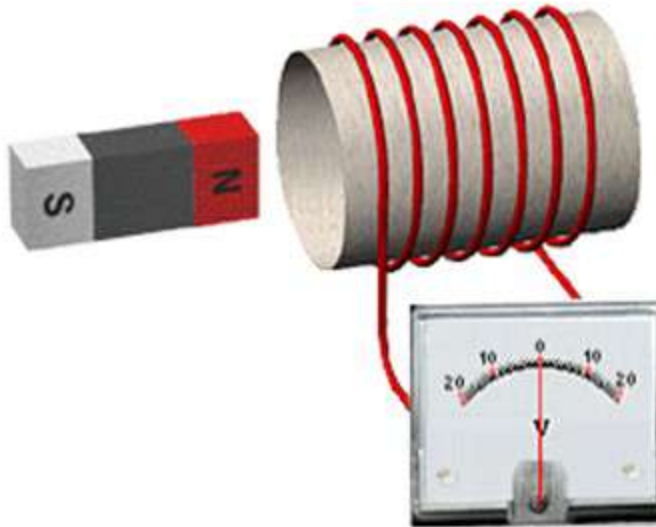

Observe the direction of pointer of the galvanometer when motion of the magnet is reversed.

Faraday's Laws of Electromagnetic Induction


- Faraday summed up the facts from his experiment into two laws known as **Faraday's Laws of Electromagnetic Induction**.

Faraday's First Law

- Whenever the magnetic flux linked with a circuit changes, an emf is always induced in it.

OR

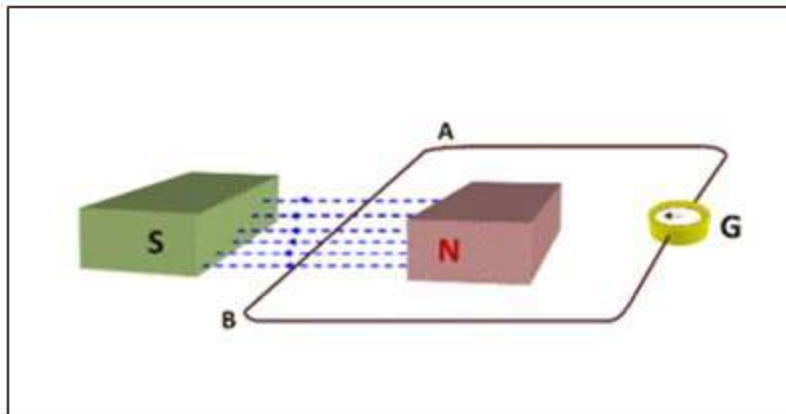- Whenever a conductor cuts magnetic flux, an emf is induced in that conductor.



Faraday's Second Law

- The magnitude of the induced emf is equal to **the rate of change of flux-linkages**.
- Suppose a coil has **N turns** and flux through it changes from an initial value of Φ_1 webers to the final value of Φ_2 webers in **time t** seconds.

Initial flux linkages = $N\Phi_1$

Final flux linkages = $N\Phi_2$

$$\text{Induced emf} = \frac{\text{Change in flux}}{\text{Time}} = \frac{N\Phi_2 - N\Phi_1}{t} \text{ Wb/s}$$


$$e = N \frac{\Phi_2 - \Phi_1}{t} \text{ volt}$$

- Putting the above expression in its differential form, we get

$$e = \frac{d}{dt}(N\Phi) = N \frac{d\Phi}{dt} \text{ volt}$$

- Usually, a **minus sign** is given to the **right-hand side expression** to signify the fact that the induced emf sets up current in such a direction that magnetic effect produced by it opposes the very cause producing it.

$$e = -N \frac{d\Phi}{dt} \text{ volt}$$

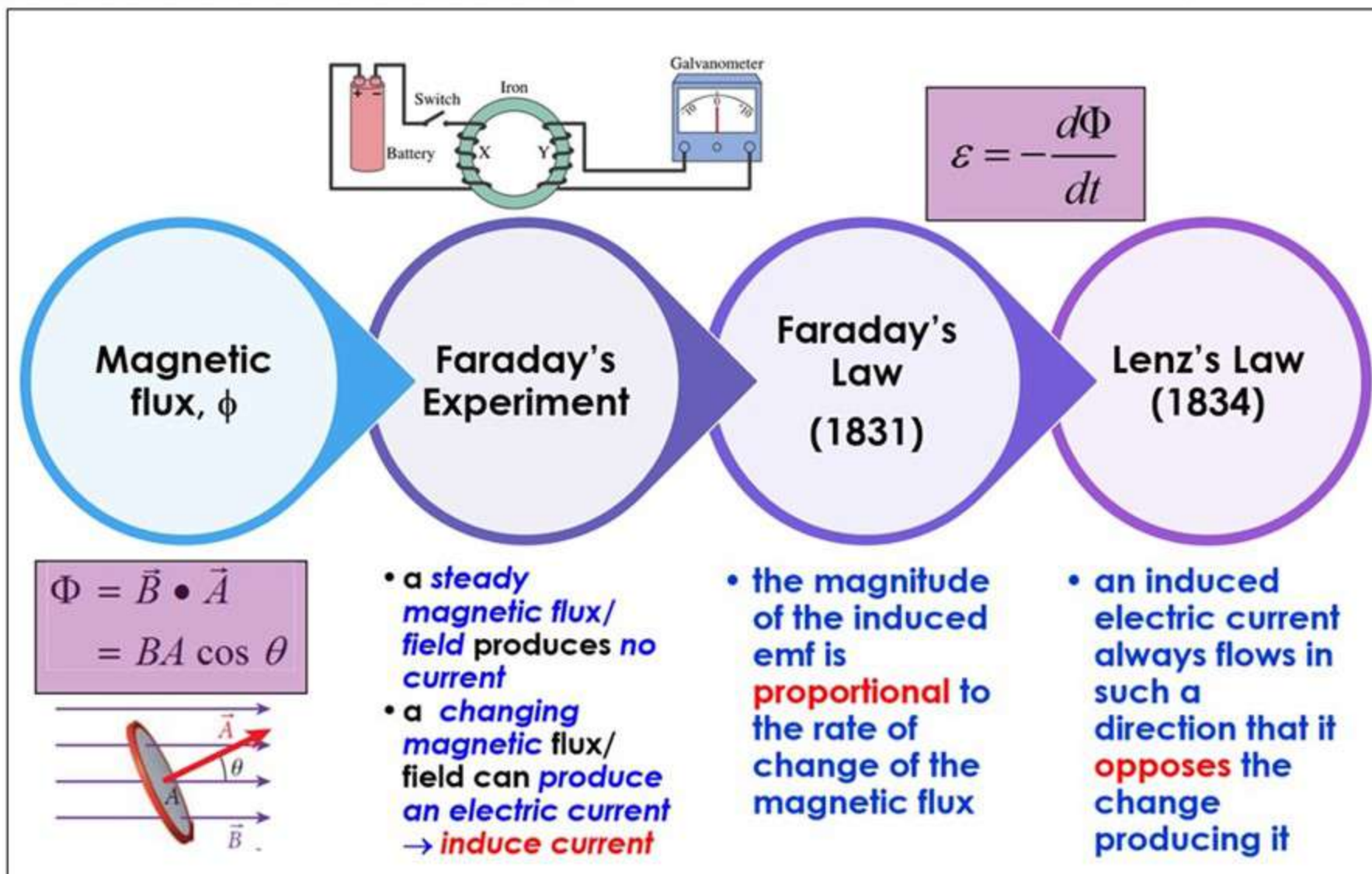

Direction of Induced emf and Currents

- There exists a definite relation between
 - ❖ the direction of the induced current,
 - ❖ the direction of the flux and
 - ❖ the direction of motion of the conductor
- The direction of the induced current may be found easily by applying either **Fleming's Right-hand Rule** or **Flat-hand rule** or **Lenz's Law**.

Fleming's Rule




Dynamically induced emf

Lenz's Law




Statically induced emf

Electromagnetism

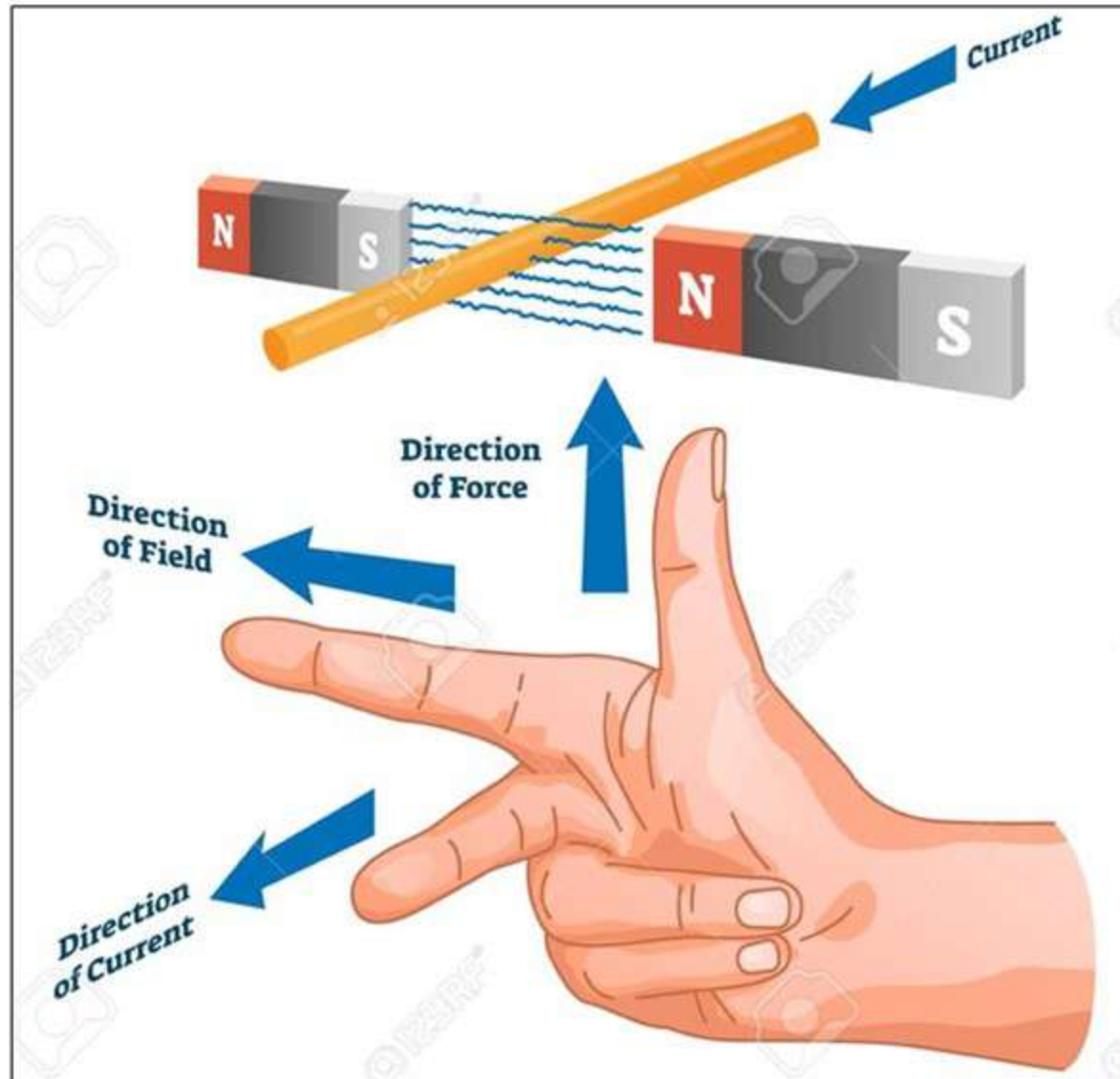

**Fleming's
Right-hand
Rule**

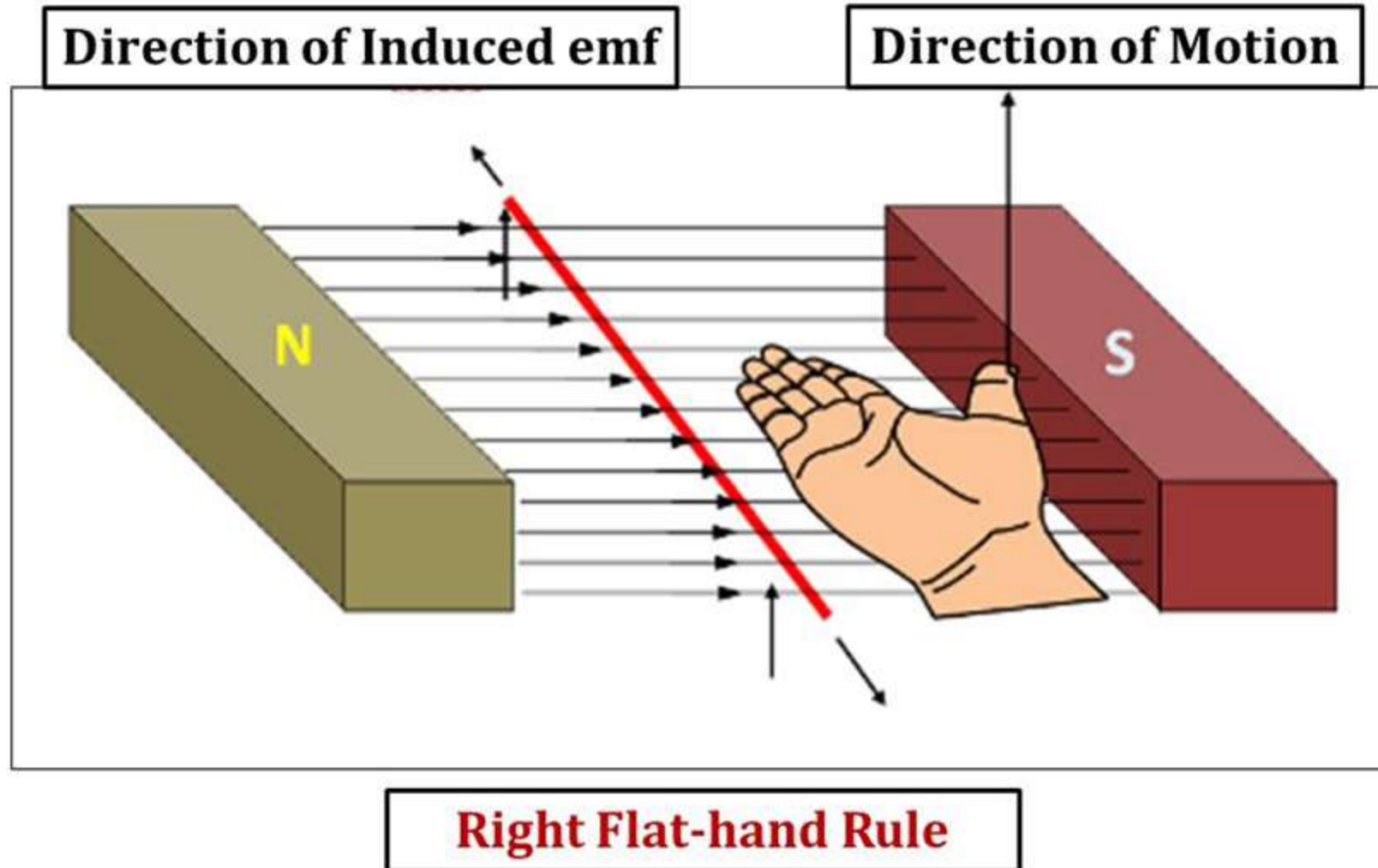

Lenz's Law

- Electromagnetically induced current always flows in such direction that the action of the magnetic field set up by it tends to oppose the very cause which produces it.

